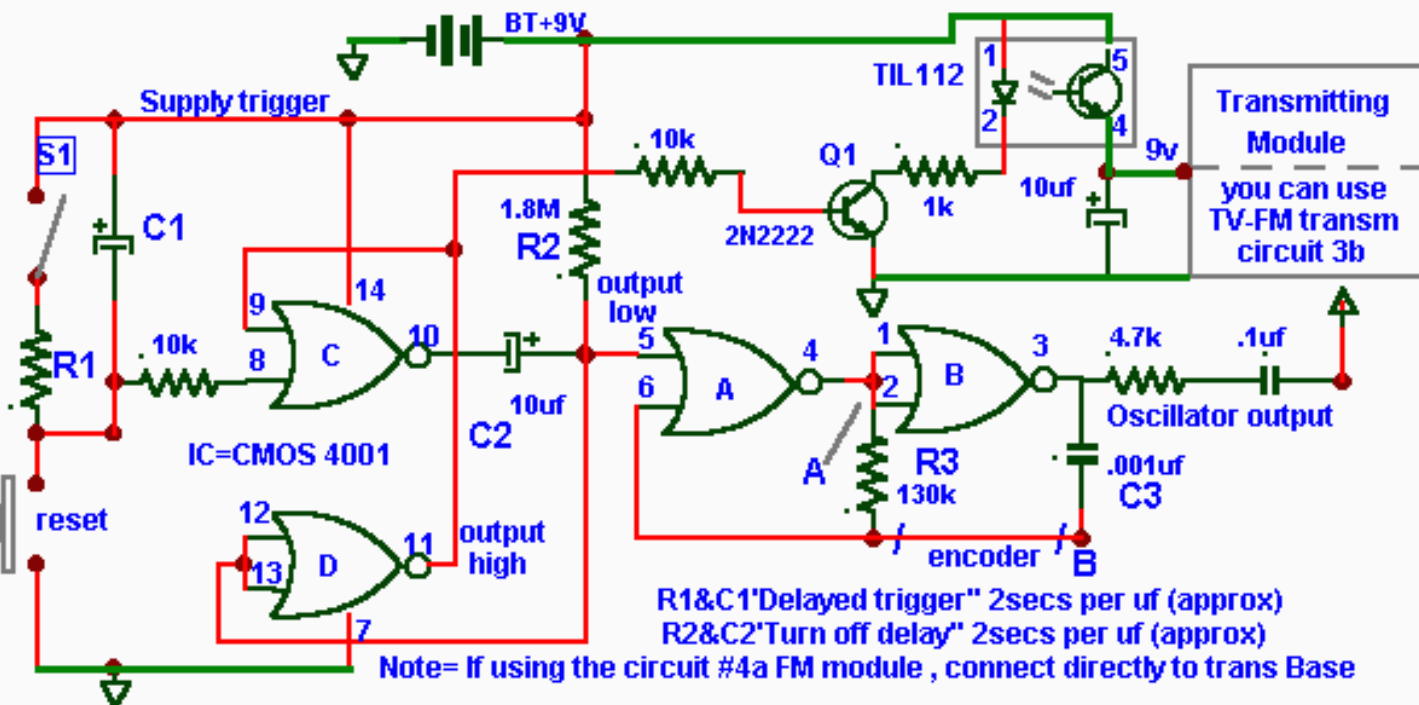


Wireless Alarm FM Transmitter Module

Designed by L.Gendron(1988)



You may decide to build several small alarm units after your success with the first one. One way of identifying each of these transmitters is assigning a different tone for each unit by changing the frequency . To do this R3 at points (A) as shown on the oscillator portion of the CD4001 (A-B) must be changed . While using a fixed capacitor C3 at point B an encoder could be substituted at A and B in series with C3 instead of the present fixed R3 . Such an encoder is shown made up with a 14 pin DIP for seven switches, actually, four would probably suffice using parallel switching for different chosen resistor values for each frequencies . On the other hand , if each transmitter would be assigned its own frequency with fixed R3/C3 this would simplify the construction and do just as well.

As for the transmitter I have used the Radio/TV FM transmitter in [#3b](#) and a small portable FM radio taking the signal from the headphones output for processing and it worked very well. The transmitter doesn't need an antenna for close range and it tunes the lower FM band around 88MHz with the variable capacitor. There are now many new types of miniature Tx/Rx modules that can be had from electronic suppliers that could be used and greatly simplify the project.


The FM "Mini- receiver" on this page could be used , R1 (PC type) controls the regeneration and after adjusting for best reception it should be locked in place with a dab of silicon as you may need to readjust it later. The 25pF variable capacitor tunes the selected frequency and R2 provides the load and must be adjusted for maximum output to an amplifier stage without distortion. Another option worth considering is the RF Detector described in Handy Dandy Little Circuit [#15b](#).

On page two I describe the application of the LM567 as tone decoder.




Handy Dandy Little Circuits #17-2

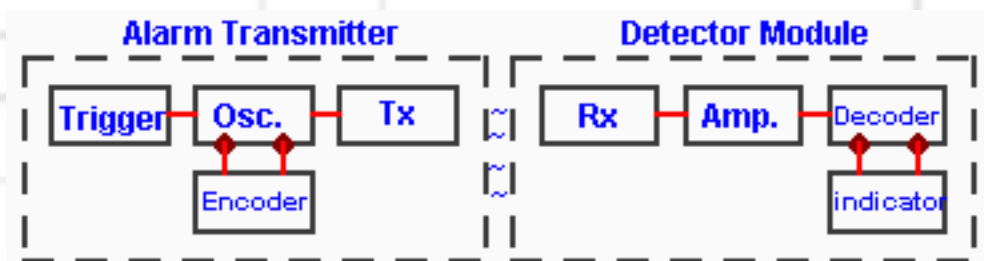On page one I detailed the Alarm Transmitter functions and said that it could be combined with an Encoder so that the encoded received signal could be decoded for Alarm identification. The following function block shows how it is combined to form a complete system.



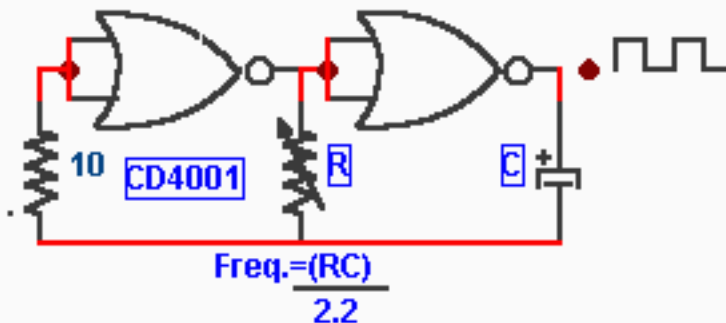Use this circuit to test with LM567
and find RC for a given freq.
At matched center freq. LED will be ON



To ease the burden of testing and finding the resistance values to use for each frequency I include a small oscillator to feed the decoder (LM567), use a 9 volts supply or battery for both units while testing.

Some points to observe


- 1- Keep R between 2K and 20K
- 2- calculate R/C so that frequencies are at least 500hz apart for a good distinctive detection.
- 3- So that we can use a fixed Cap. C and enable you to change only the R value use freq. below 50khz.

After assembly of the test oscillator and decoder select the lowest frequency you want

to use and calculate R/C for the values to be used for the decoder and install C . Next calculate R/C for the oscillator for the exact same frequency but use a variable resistor for R within the found values and install . Thereafter you may use the fixed capacitor values for the oscillator and decoder within the frequencies limit you want to use.

Next with a scope or a frequency counter check that the oscillator is working and adjust R to obtain the frequency you want . Turn power off and measure the resistance of R and make note of it with the freq . Do not readjust R . Connect the oscillator to the decoder input, turn the feed-back gain resistor R1 (100K) of the op-amp to one third , turn power on , if you have a scope check for a signal (square wave) at the op-amp output and adjust amplification for a good signal (~ 5vdc) then slowly vary the detector resistance R while observing that the LED turns on , STOP right there and measure the detector R and make note of the resistance value at the time the LED is turned on.

Next ,assuming you already have built your first alarm transmitter module and it is working apply the same values of R/C with the closest standard fixed value for "R" as found for the test oscillator to the alarm oscillator. Disconnect the test oscillator from the detector and with a common power supply to the alarm module and the detector use a jumper from the alarm oscillator output and connect to the decoder input and fire up the circuits. If the LED does not turn on readjust first R1 then the detector R until it does and lock in place with a dab of silicon .

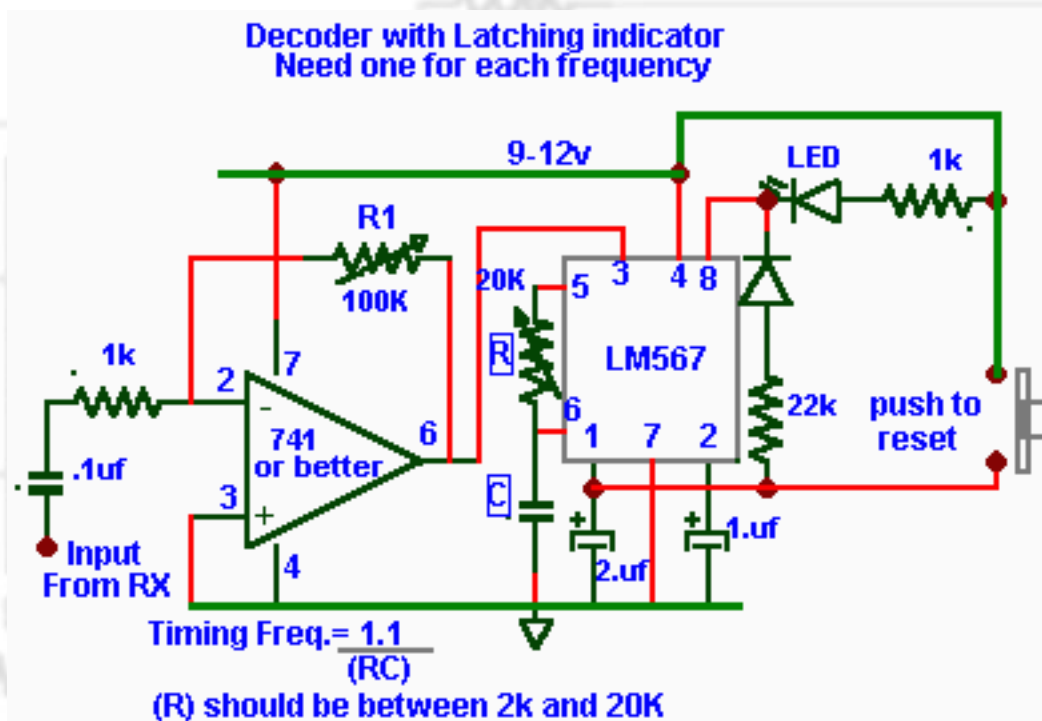

P.S. The frequency for the above decoder with values of R = 10K and C = .1uF is 110Hz.

[Back to Page #1](#)

[See page #3 for PC layouts](#)



Handy Dandy Little Circuits #17-3

FM Receiver

You could use a small FM receiver for convenience taking the output signal from the headphone connector connected to an external volume control (about 10K ohms) then to the decoder.

If you have something smaller in mind then the following FM receiver can be constructed with the TDA7000 IC which is still available from some distributors . No special skill is required except care must be taken that all the capacitors all wired as close as possible to the pins. The recommended supply voltage is 4.5 volts but up to 9 volts can be used .



The coil (L1) is made of 6 turns of # 20 insulated wire on a 1/4 " form . Tuning is simple enough once you have your transmitter operating simply tune the variable capacitor with a non-metallic screw driver very slowly until the signal is detected anywhere on the FM band .

The signal output is very small , only suitable for crystal headphone and must be amplified if you want to hear it . The LM386 amplifier is well suited for that purpose .

See [LM386](#)

Parts list

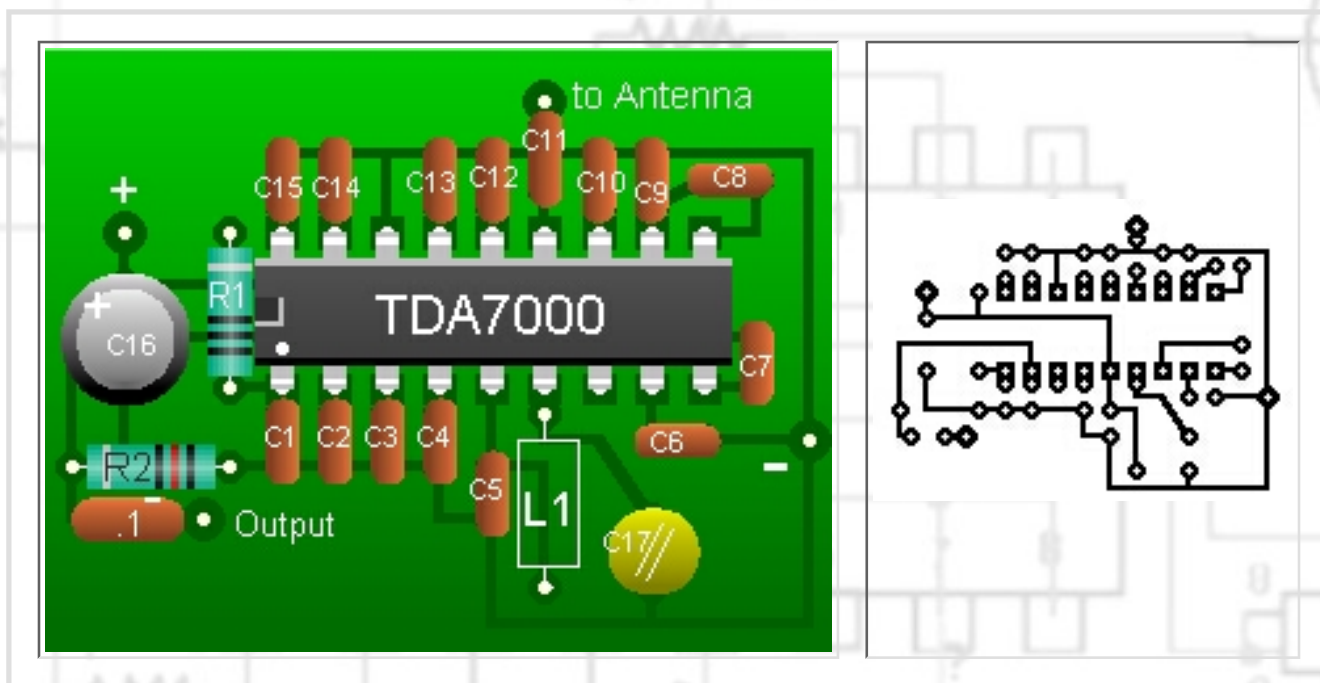
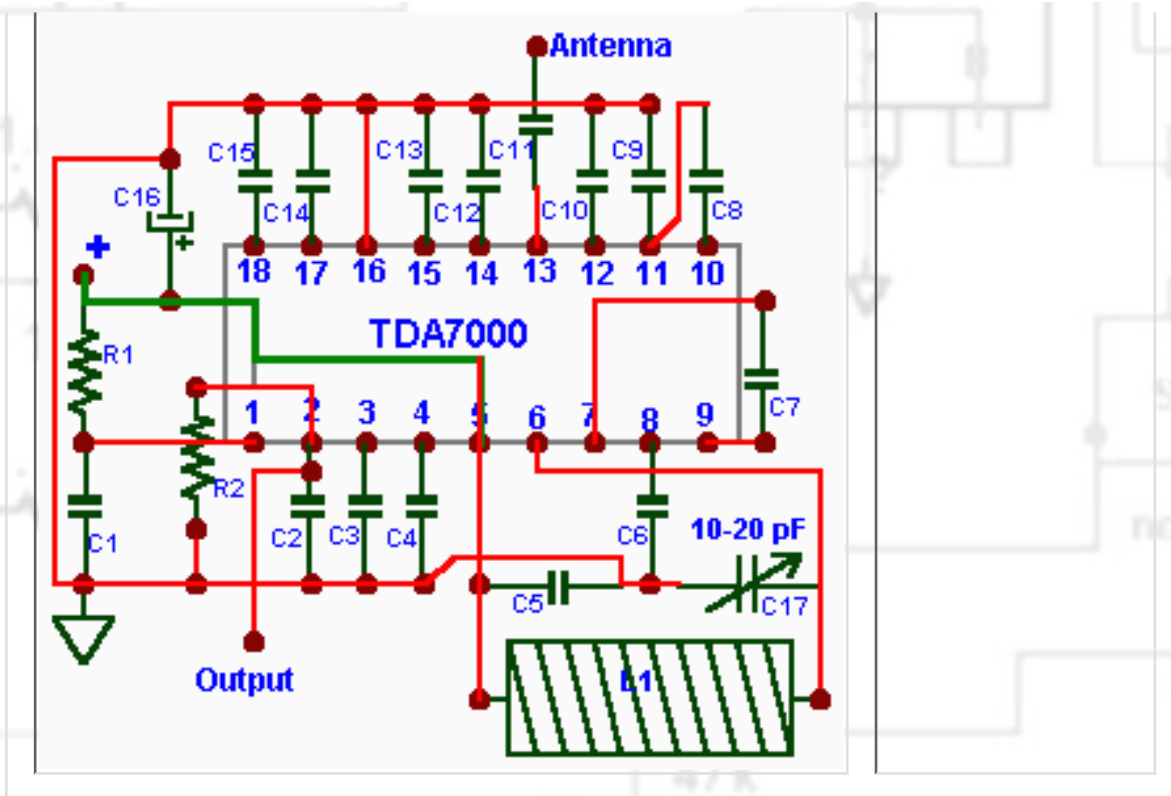
C1 = .15 uF
 C2 = .002 uF
 C3 = .022 uF
 C4 , C5 = .01 uF
 C6 = 180 pF
 C7 , C9 = .003 uF
 C8 , C14 = 330 pF
 C10 = 150 pF
 C11 = 100 pF
 C12 , C15 = 220 pF
 C13 = .1 uF
 C16 = 47 uF /15v
 C17 = 10 -20 pF Var.
 R1 = 10K
 R2 = 22K
 L1 = see text





Layouts and PCBs

The following shows PC layouts for each circuits on page one and two. For clarity the PCB layouts are illustrated about twice the size than the actual PC board would be. On a standard perforated board , point to point wiring using #24 size wire or smaller can be used with the same layout instead of a printed circuit board .



Detecting Module

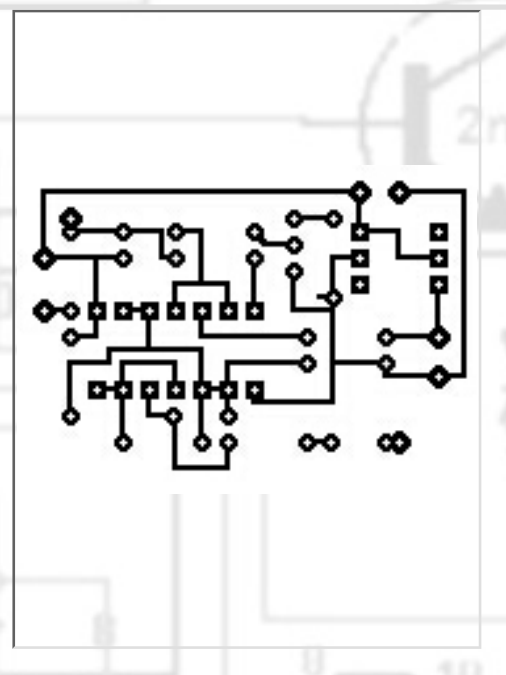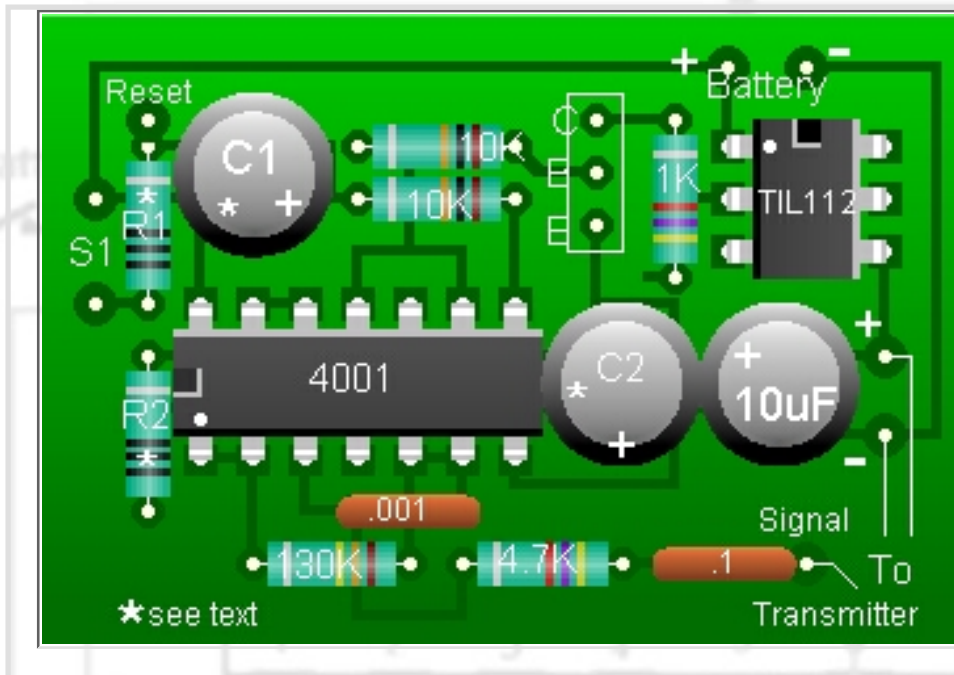

Decoder Module

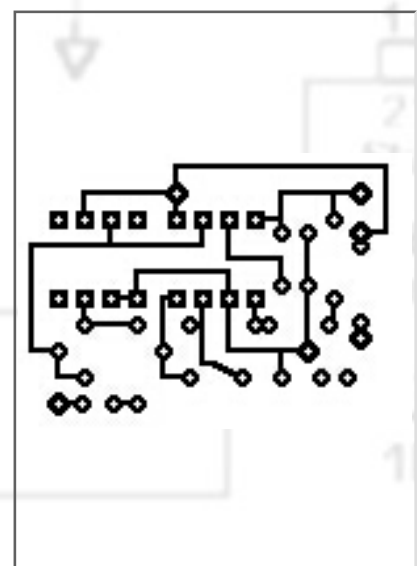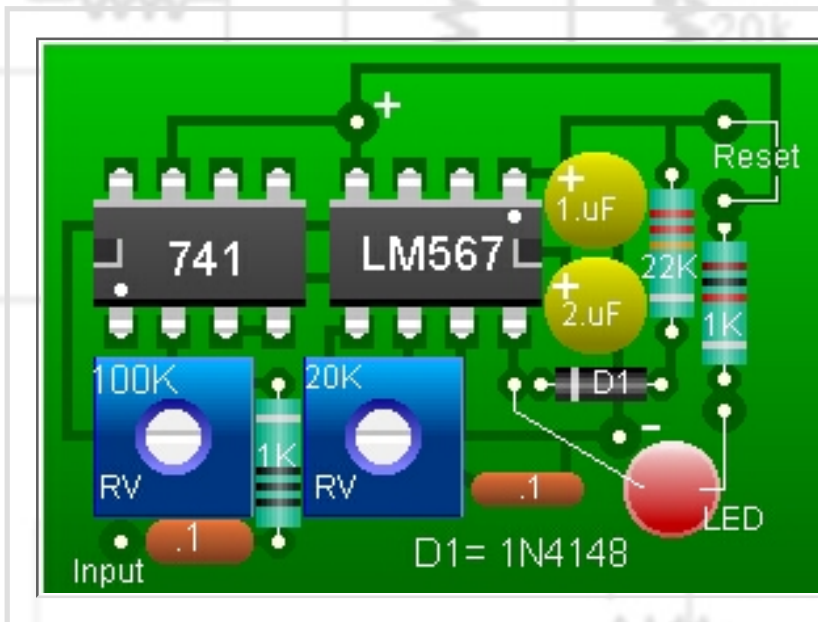

FM Transmitter Module

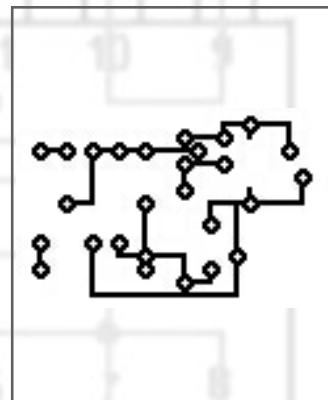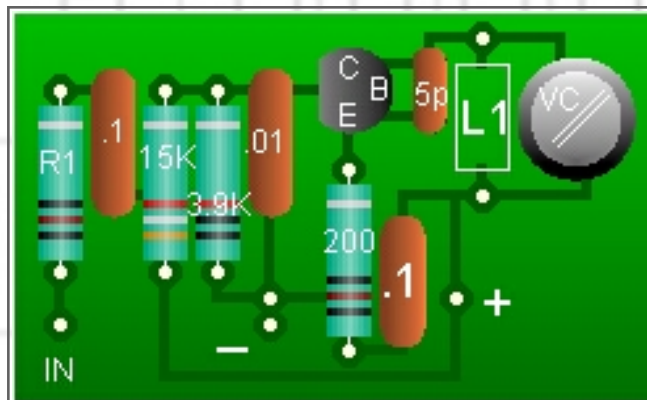

[Back to Page #1](#)

[Back to Page #2](#)

[Home](#)

Questions? Email me at roma60@home.com

© Laurier Gendron, Burnaby, B.C., Canada. 1999/mg

