

Edited by Bill Travis

Calibrate scope jitter using a transmission-line loop

David Cuthbert, Micron Technology, Boise, ID

DIGITAL-CLOCK-PERIOD JITTER is the variation in the period of a clock cycle compared with a nominal (average of many cycles) clock period. To accurately measure period jitter using an oscilloscope, you must subtract the oscilloscope jitter from the measured jitter. However, oscilloscopes rarely have a jitter specification, so you must determine the oscilloscope jitter. One method of measuring oscilloscope jitter is to use the oscilloscope to measure the jitter of a pulse generator with known jitter. The measured jitter, assuming the jitter has a Gaussian distribution, is $\sqrt{(\text{scope jitter})^2 + (\text{generator jitter})^2}$. Rearranging the formula to solve for oscilloscope jitter, the scope jitter is $\sqrt{(\text{measured jitter})^2 - (\text{generator jitter})^2}$. The ideal generator for measuring oscilloscope jitter would have zero jitter. **Figure 1** is a circuit for generating a calibration signal with near-zero timing jitter.

A transmission-line delay loop creates a delayed pulse at the oscilloscope. **Figure 2** shows the circuit in operation. You set the oscilloscope for internal trigger-

 


Figure 1

You can use a transmission-line delay loop to accurately measure an oscilloscope's jitter.

ing on the first pulse and then configure the scope to measure the time between the first pulse and the delayed pulse. You set the trigger hold-off such that the oscilloscope always triggers on the first pulse. The second pulse in each set of pulses is the first pulse delayed through the transmission-line delay loop. Two 50Ω coaxial transmission lines implement the circuit and connect to the oscilloscope using two BNC T adapters. The line from the 50Ω generator to the 50Ω oscilloscope can be of any length. The length of the delay-loop line determines the delay between the first pulse and the delayed pulse. You set the generator's pulse period to approximately five times the loop delay and the generator's pulse duration to approximately one-half the loop delay.

The waveforms in **Figure 2** represent a pulse period of 62 nsec and a pulse duration of 6 nsec. The delay loop consists of 2.4m of RG-58 coax and creates a delayed pulse 13 nsec after the first pulse. The 13-nsec delay is equivalent to calibrating the oscilloscope with a zero-jitter, 77-MHz signal. The impedance relationships are such that the delayed pulse has

the same amplitude as the first pulse. With the 50Ω pulse generator set for 1V into 50Ω, the generator sends a 1V incident pulse toward the oscilloscope. As the incident pulse "sees," the node at the oscilloscope consists of the 50Ω scope in parallel with the two 50Ω ends of the delay loop. Therefore, the impedance at this node is 16.7Ω, and the reflection coefficient is -0.5 . The impedance mismatch causes a pulse amplitude of 0.5V to appear at the oscilloscope and a reflected pulse of $-0.5V$ to travel to the generator, where it dissipates. Two 0.5V pulses travel in opposite directions through the delay loop and meet 13 nsec later at the oscilloscope, forming a 0.5V pulse with a source impedance of 25Ω.

The 50Ω oscilloscope, in parallel with the 50Ω line to the generator, forms a 25Ω load that matches the 25Ω pulse source impedance. The delayed-pulse amplitude at the oscilloscope is 0.5V, and a 0.5V pulse travels to the pulse generator, where it dissipates. You can analyze the circuit's action by keeping track of where the energy goes. The 1V generator sends a 20-mW pulse down the 50Ω line. When this pulse encounters the oscilloscope and delay loop, the energy splits four ways. In this split, 5 mW reflects back to the generator where it dissipates, 5 mW dissipates in the oscilloscope, and 5 mW enters each end of the delay loop. When the two 5-mW pulses exit the delay loop, 5 mW dissipates in the oscilloscope and 5 mW travels to the generator, where it dissipates. You can calibrate several oscilloscopes and one pulse generator with the delay loop. Because the loop has near-zero jitter, the jitter that an os-

Calibrate scope jitter using a transmission-line loop	97
Excel offers painless LCD initialization	98
Microcontroller selects minimum/maximum value	100
Circuit forms industrial-grade digital potentiometer	104
Passive filter cleans up power-line communications.....	106

illoscope measures is virtually all oscilloscope jitter. The loop allowed a generator with 19-psec rms jitter to calibrate an oscilloscope having 3.8-psec jitter.

Figure 2

The delay loop has some jitter, created by the conversion of amplitude noise to jitter. Without the loop, generator-amplitude noise causes the leading edge of each pulse to cross the oscilloscope's trip point either early or late. In this way, amplitude noise translates to jitter. The following formula gives jitter versus amplitude noise:

$$\text{JITTER} = \frac{\text{AMPLITUDE NOISE}}{dV/dt}$$

An ideal loop would produce a delayed pulse that is identical to the first pulse. Amplitude noise on the delayed pulse would be identical to that on the first pulse; thus, jitter attributable to the noise would cancel out. Because of signal loss in a real loop, the delayed pulse is not identical to the first pulse. Therefore, the amplitude noise of the delayed pulse will be less than that on the first pulse, and a conversion of amplitude noise to jitter will occur. The following formula gives amplitude noise versus jitter in the loop:

$$\text{LOOP JITTER} = \frac{\text{AMPLITUDE NOISE}}{dV/dt} \times (\text{SIGNAL LOSS})$$

The pulse generator used to calibrate the oscilloscope exhibits 250 μV of rms noise and a dV/dt of 0.35V/nsec. The sig-

nal loss on the leading edge of the delayed pulse is 0.2V. The amplitude-noise-to-jitter conversion is thus:

$$\text{LOOP JITTER} = \frac{250 \mu\text{V}}{0.35\text{V/nSEC}} \times (0.20) = 143 \text{ fSEC.}$$


The loop jitter of 145 fsec is so far below the jitter noise floor of the oscilloscopes under calibration that you can consider the delay loop as a zero-jitter source. Because digital-oscilloscope jitter is a function of the timebase setting and

the amount of ADC dynamic range you use, you should calibrate the scope with a loop delay and amplitude that match the signal to the actual system or device under test.

REFERENCE

 1. Adler, Joe, "Jitter in clock sources," Application Note, Vectron International.

Is this the best Design Idea in this issue? Vote at www.ednmag.com.




The transmission-line delay loop creates a delayed signal with near-zero jitter for calibrating the oscilloscope.

Excel offers painless LCD initialization

Alberto Bitti, Eptar, Lugo, Italy

TO DISPLAY A FONT or a symbol on an LCD, you need to convert the desired character into numerical data. Creating the data for an entire font set requires specialized tools; even with these tools, the task can be daunting. Alternatively, you can build a font calculator using an Excel spreadsheet. This technique takes advantage of the tabular nature of a spreadsheet to automatically create the required initialization code. The example in **Figure 1** applies to displays arranged in blocks comprised of eight pixels by

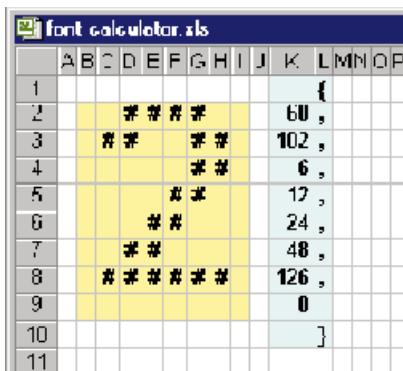

eight pixels. You can easily adapt it to any other arrangement, such as the seven-by-five-pixel format used in the eight customizable characters found in most alphanumeric displays. Cells inside the yellow area represent the symbol "pixels." You draw the desired font character or symbol using a bold character such as "#." The formula in **Figure 2** is all that

Figure 1 You edit the graphical shape (yellow). A simple formula builds the initialization code (blue), which is ready to paste in your application.

you need to obtain the initialization data. For each of the eight pixels in a row, the formula tests whether the pixel is blank (LEN is zero); otherwise, it adds the pixel's "weight" (1, 2, 4, 8, 16, 32, 64, or 128) to the result.

You can prepare the spreadsheet in minutes. Type the formula in the first position (K2), then copy it to all eight rows in a symbol (the blue area from K3 to K9). Complete it with the separators for your language of choice (commas and parentheses for C). To build an entire character set, copy the whole block as many times as necessary. To edit the fonts, place the cursor over the cells and

Figure 2

```
= IF ( LEN ( B2 ) ; 128 ; 0 ) +
  IF ( LEN ( C2 ) ; 64 ; 0 ) +
  IF ( LEN ( D2 ) ; 32 ; 0 ) +
  IF ( LEN ( E2 ) ; 16 ; 0 ) +
  IF ( LEN ( F2 ) ; 8 ; 0 ) +
  IF ( LEN ( G2 ) ; 4 ; 0 ) +
  IF ( LEN ( H2 ) ; 2 ; 0 ) +
  IF ( LEN ( I2 ) ; 1 ; 0 )
```

The formula (which, in this example, shows cell K2) adds pixel "weights" to obtain initialization values.

type "#" (or any other character), and use "Canc" to delete. After editing, select all

of the columns K and L; then cut and paste the code into your application. Besides saving you money, this technique is convenient and flexible. You can adapt it in minutes to any language (useful when you switch between assembly dialects). Moreover, the method accommodates useful additions, such as inserting #define KEY_ICON to name a particular data set, to suit your application's requirements.

Is this the best Design Idea in this issue? Vote at www.ednmag.com.

Microcontroller selects minimum/maximum value

Abel Raynus, Armatron International, Melrose, MA


MICROCONTROLLER-BASED SYSTEMS for measurement, sensor-data processing, or control, sometimes require you to determine a maximum or minimum data value. For example, in an object-detection system, such as a radar or sonar system, the microcontroller receives echo signals from multiple targets and then must select the closest one; in other words, it must determine the minimum distance. Another example is an

automatic-tuning system in which the microcontroller acquires data and must determine the maximum or minimum values of the data. A simple way to determine maximum and minimum value involves a microcontroller, IC₁, that receives a set of data from N sources (Figure 1). The data should be in 8-bit format. To simplify the process, consider that the data are 1-byte-long integers. In other words, the data cover the range 0 to 255.

In most cases, this range produces satisfactory results. The same limitation applies to the number of data sources. If you need more data precision or more data sources, then you can use two or more bytes at the expense of added program complication.

Two approaches exist for the maximum/minimum values. In the first, the microcontroller memory collects the received data and processes the data to de-

Figure 1

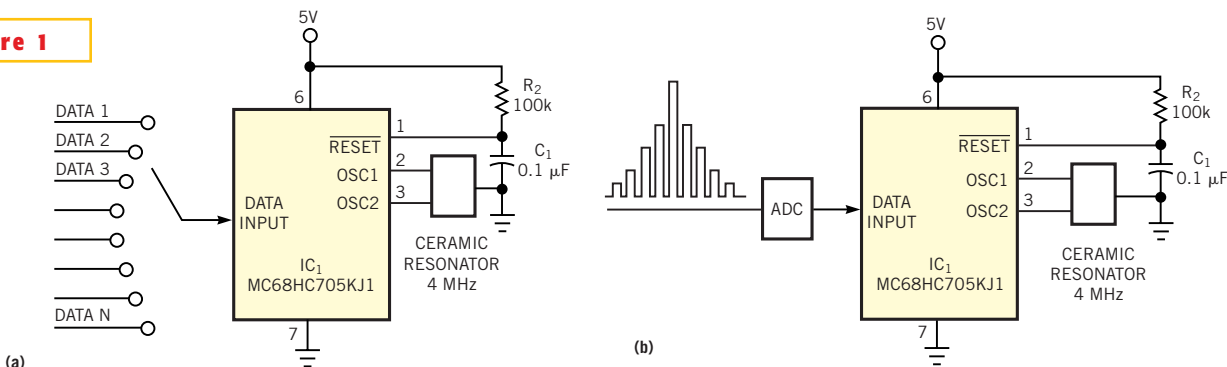

In one approach to determining minimum and maximum values, the microcontroller stores data values in memory before processing them (a); in another approach, it processes data on the fly (b).

termine maximum or minimum values (Figure 1a). In the second approach, the microcontroller processes the data immediately after receiving it (Figure 1b).

Listing 1 shows the program for the first approach. Assume that a data array with $N=8$ exists in the microcontroller's memory. For demonstration purposes, Listing 1 illustrates this part of the routine in lines six to eight and 17 to 21, in which the controller loads the data registers from a predetermined table. In a real situation, you would load the data registers from data sources before calling the program. The process of minimum-value detection is based on a method called "the bubble." The search algorithm starts testing the memory data array from its end. It clears the index register (X) after completion of the program. If you need to detect the maximum instead of the minimum value, you need change only one instruction in line 28.

In the second approach, the microcontroller waits for a data value entering the data register and, upon reception, starts processing the value (Listing 2). This approach needs no memory array. This variant of the program adds two features: First, it simultaneously selects minimum and maximum values of the incoming data and saves them in the DATAmIn and DATAmAx registers. Second, the routine considers a data value equal to 0 as no data. Thus, the data range is from 01_h to ff_h . For this project, you can use the inexpensive, one-time-programmable MC68HC705KJ1 from Motorola (www.motorola.com). Thus, the programs use Motorola's assembly language. However, the algorithms are so straightforward, they're amenable to any language and to practically any microcontroller. Go to the EDN Web site www.ednmag.com for an electronic version of the listings.

Is this the best Design Idea in this issue? Vote at www.ednmag.com.

LISTING 1—MEMORY-BASED MINIMUM/MAXIMUM DETERMINATION

```

0000
0000
07C8
07C8      03040502
          080E0919

00C0
00C0
00C8
0300
0300 [05] 3FC8
0302 [03] 5F

0303 [05] D607C8
0306 [05] E7C0
0308 [03] 5C
0309 [02] A308
030B [03] 26F6

030D [02] AE07
030F [04] E6C0
0311 [04] B7C8
0313 [03] 5A
0314 [04] E1C0
0316 [03] 2504
0318 [04] E6C0
031A [04] B7C8
031C [03] 5D
031D [03] 26F4
031F [02] 8E

07FE
07FE      0300

1 ***** MIN VALUE SELECTION VAR 1 *****
2 *nolist
3 $include "std-j1a.asm"
4 *list
5 *****
6 tabl equ ROMend-$07 ;for demo only !
7   org tabl      ;table of Data
8   fcb 3,4,5,2,8,14T,9,25T

9 *****
10  org RAM
11  DATA      rmb 8
12  DATAmIn   rmb 1
13  org ROM
14  start clr DATAmIn
15  clrX
16 *****
17 m0 lda tabl,x ;put the set of data from
18   sta DATA,x ;table to registers. This
19   incx      ;part of program only for
20   cpx #8    ;the idea demonstration.
21   bne m0
22 *****
23   ldx #7    ;N-1 into X-register
24   lda DATA,x ;data8 into Acc.
25   sta DATAmIn ;store data8 in DATAmIn
26   mn0 decx  ;go to the next data,x
27   cmp DATA,x ;if DATAmIn < DATA,x
28   blo mn1   ; then go to mn1
29   lda DATA,x ;otherwise replace DATAmIn
30   sta DATAmIn ; with new data value
31   mn1 tstx ;if there are more data to be tested,
32   bne mn0   ; then repeat from mn0
33   stop     ;end of the program
34 *****
35   org VECTORS+6
36   fdb start
    
```

LISTING 2—ON-THE-FLY MINIMUM/MAXIMUM DETERMINATION

```

*****
0000
00C0
00C0
00C1
00C2
0300
0300 [02] A6FF
0302 [04] B7C1
0304 [05] 3FC2
0306 [05] 3FC0
0308 [03] 5F

0309 [03] B6C0
030B [03] 27FC
030D [03] B1C1
030F [03] 2402
0311 [04] B7C1
0313 [03] B1C2
0315 [03] 23F2
0317 [04] B7C2
0319 [03] 20EE

07FE
07FE      0300

1 ***** MIN/MAX VALUE SELECTION VAR 2
2 *nolist
3 $include "std-j1a.asm"
4 *list
5 *****
6   org RAM
7   DATA      rmb 1
8   DATAmIn   rmb 1
9   DATAmAx   rmb 1
10  org ROM
11  init lda #$ff
12  sta DATAmIn
13  clr DATAmAx
14  clr DATA
15  clrX
16 *****
17 start lda DATA ;wait for DATA / 0
18   beq start
19   cmp DATAmIn ; Data > DATAmIn?
20   bhs m0
21   sta DATAmIn
22   m0 cmp DATAmAx ; Data < DATAmAx?
23   bls start
24   sta DATAmAx
25   bra start
26 *****
27   org VECTORS+6
28   fdb init
    
```

Circuit forms industrial-grade digital potentiometer

Phill Leyva, Maxim Integrated Products, Sunnyvale, CA


BOTH AC AND DC MOTORS in modern industrial systems often receive their control from PLCs (programmable-logic controllers) in a control room safely away from the process. If an operator must manually set the motor speed while observing the process, the component of choice is usually an industrial-grade potentiometer. The wiper of this potentiometer produces a signal of 0 to 10V that feeds back to a motor controller in the control room. Such potentiometers are expensive and prone to wear, however. Because of wear, they can open the control loop, allowing the motor to ramp up uncontrollably. With a few components, you can implement a reliable, low-cost, surface-mount digital potentiometer for industrial applications (Figure 1). The result is a direct drop-in replacement for the wear-prone mechanical potentiometer. The digital potentiometer occupies the same space as a

mechanical unit within an enclosure. It takes power from the 10V that is formerly supplied to the mechanical potentiometer from the motor controller. The solid-state unit provides a similar output of 0 to 10V and delivers as much as 15 mA to the controller.

The key to the circuit is the low-power, digital-potentiometer 100-k Ω IC₃. Configured as a voltage divider, this IC provides an output of 32 discrete voltage steps between its minimum and maximum settings (0 and 5V). A low-power linear regulator, IC₁, provides a 5V supply rail for IC₂, IC₃, and a resistor ladder internal to IC₃. PB₁ and PB₂ constitute a double-pushbutton industrial switch. Each high-to-low transition that PB₁ produces increments the digital potentiometer's "wiper" by one step. Depressing PB₂ while toggling PB₁ decrements the wiper by one step. IC₂ is a switch debouncer that provides (in addition to the

debouncing) a 40-msec fixed delay between its outputs and the switch action. To provide 0 to 10V outputs as required by the motor controller, a single-supply, rail-to-rail op amp, IC₄, amplifies IC₃'s output by a factor of two. The input common-mode range for this op amp—250 mV beyond either supply rail—allows it to generate 0 to 10V outputs like a mechanical potentiometer. The circuit's low quiescent current ranges from 86 μ A for a 0V output to 186 μ A for a 10V output. To even further lower this quiescent current, you can choose the 200-k Ω version of IC₃. Because the op amp is stable with any capacitive load, it easily drives long, shielded, multiconductor cable lines back to the control room.

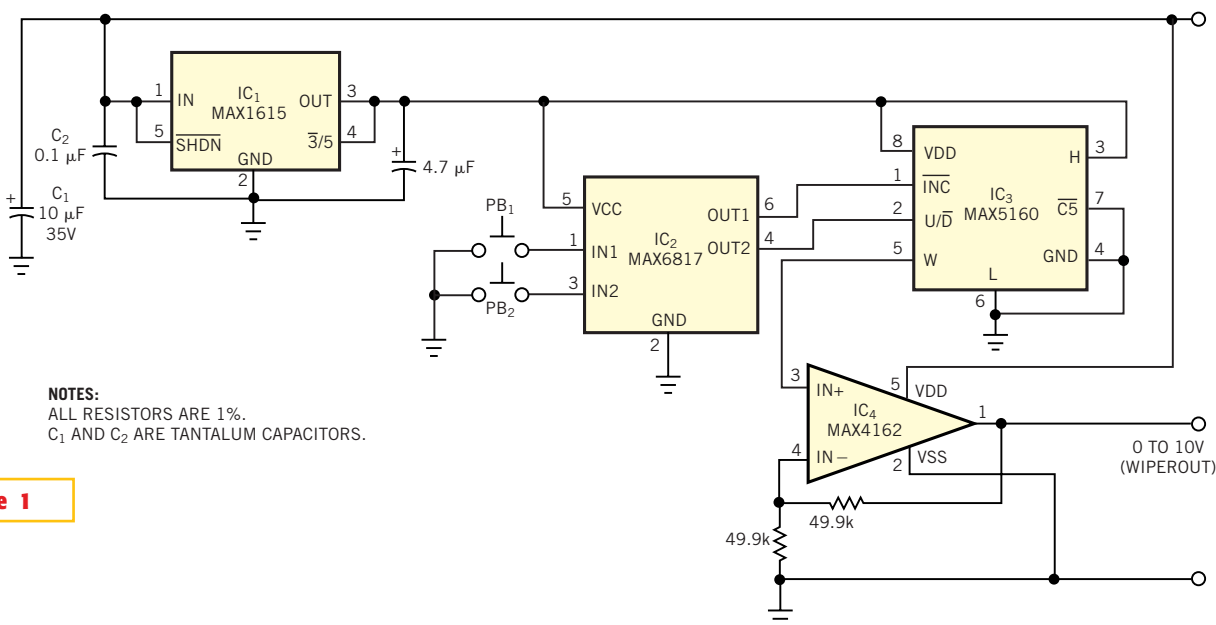Is this the best Design Idea in this issue? Vote at www.ednmag.com.



NOTES:
ALL RESISTORS ARE 1%.
C₁ AND C₂ ARE TANTALUM CAPACITORS.

Figure 1


This solid-state potentiometer simulates a mechanical potentiometer and fits in the same space.

Passive filter cleans up power-line communications

Jose Sebastia and JJ Perez, Polytechnic University of Valencia, Spain


MANY APPLICATIONS require the design of custom analog filters (Reference 1). The application for this design required simple and low-cost I/O filters for PLC (power-line communications), where low power consumption is a crucial factor. **Figure 1** shows the filters, which use passive components because of the requirement for low power consumption. The PLC system needs an in-

Figure 2

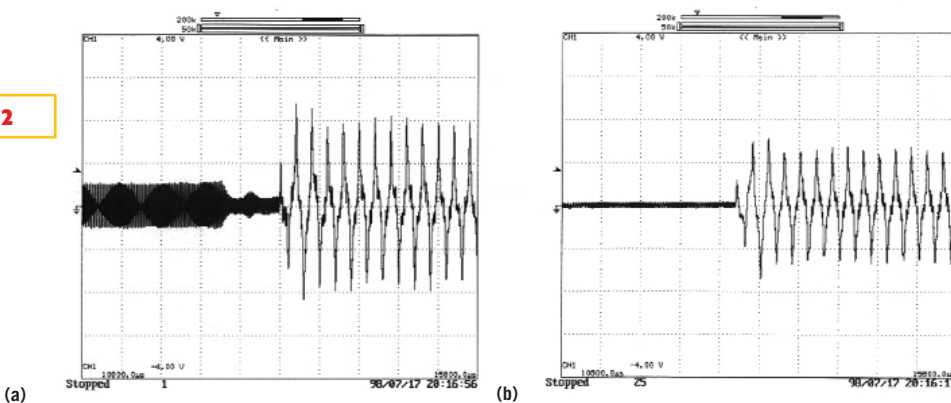

Without an input filter, a great deal of hash accompanies the input signal (a); the addition of the filter considerably cleans up the signal (b).

Figure 1

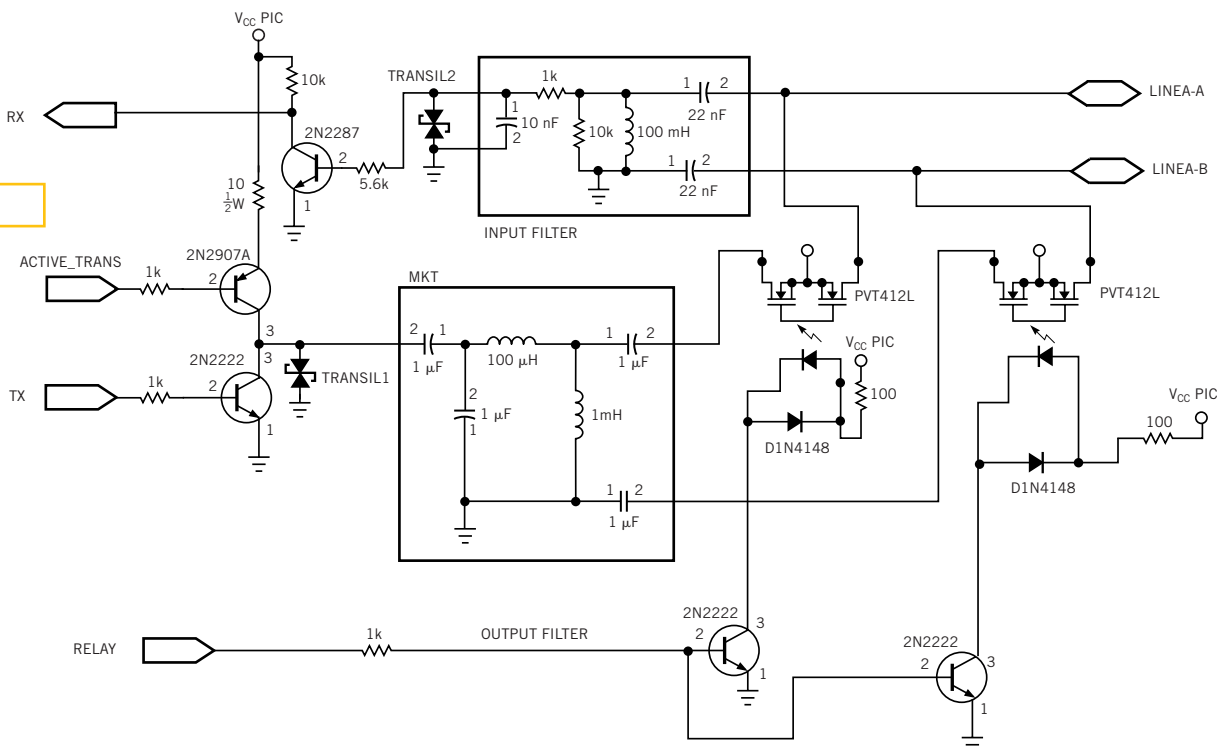

A power-line-communications system needs input and output filters to eliminate interference.

put and an output filter. They are 100-Hz to 20-kHz passband filters; the communication frequency is 5 kHz. The difference between the two filters lies in the input impedance. The input filter must present a 2.2-k Ω impedance, and the output filter must have a 30 Ω impedance. The circuit also needs a solid-state relay, the PVT412 from International Rectifier (www.irf.com) to isolate the output filter.

When the circuit is active, the relay connects the output filter to the line. A microcontroller controls the relay to implement the signal-transmission and -reception protocols. ACTIVE_TRANS, RELAY, and TX are the microcontroller pins that control transmission, and RX is the pin that controls reception. **Figure 2**

shows waveforms before (**Figure 2a**) and after (**Figure 2b**) insertion of the input filter. **Figure 3** shows waveforms before (**Figure 3a**) and after (**Figure 3b**) insertion of the output filter.


REFERENCE

1. Lacanette, Kerry, "A basic introduc-

tion to filters: active, passive, and switched-capacitor," Application Note AN-779, National Semiconductor, 1991.

Is this the best Design Idea in this issue? Vote at www.ednmag.com.

Figure 3

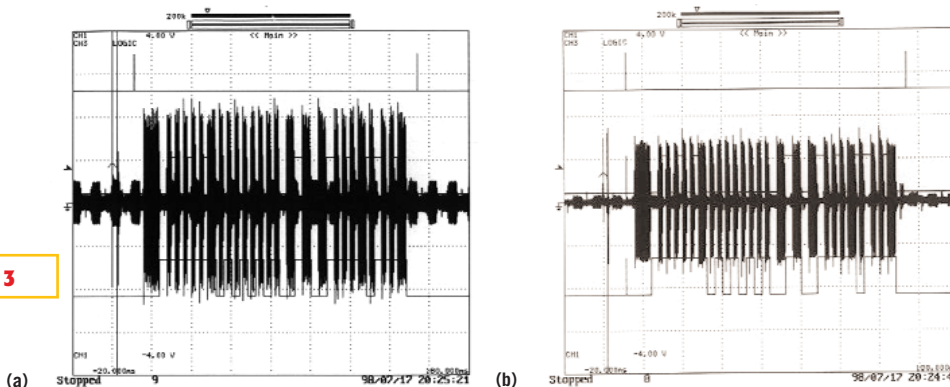

Interference and noise are evident in the output signal (a); the addition of the output filter (b) markedly reduces the noise.