



Figure 1

A low level at the outputs of IC_{1D}, IC_{1E}, and IC_{1F} activates the piezo-buzzer and warns of ac-line failure.