



**Figure 1**

**This N+1 divider displays no decoding spikes, even at high clock rates. The added NOR circuit ensures proper start-up.**