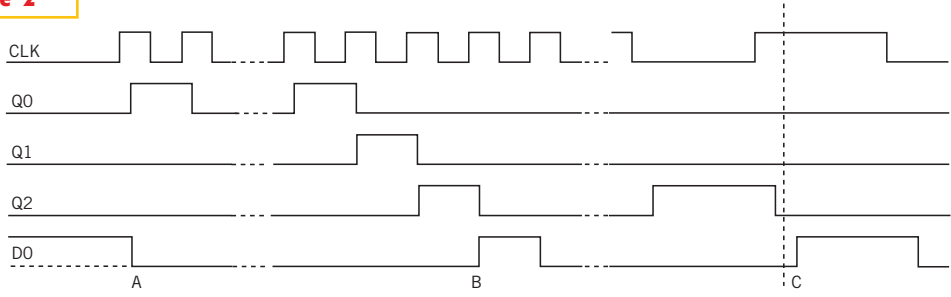


Figure 2



These waveforms illustrate the operation of the N+1 divider; note the propagation delay from the NOR gate in Section C.