



Figure 2

With the addition of six diodes, you can cascade two first-event detectors.