



Figure 1

This first-event-detection circuit uses standard 74F74 flip-flops with a 5V supply.