

Edited by Bill Travis and Anne Watson Swager


## Equal-element filter improves passband performance

Richard M Kurzrok, RMK Consultants, Queens Village, NY

**D**ESIGNERS ORIGINALLY conceived equal-element filters as all-pole microwave bandpass filters that provide minimum center-frequency insertion losses for specific values of resonator-unloaded Q (**Reference 1**). All resonators of the equal-element bandpass filter operate at the same loaded Q. For LC filters, the equal-element filter has another advantage. In the lowpass prototype, all inductors have the same value, and all capacitors have the same value. This minimum number of circuit elements provides design simplicity and reduces filter cost.

However, the equal-element filter's response shape has one severe shortcoming. Passband amplitude ripples, due to reflection, are unacceptable for some applications. In minimum-phase-shift filter circuits, group-delay ripples that preclude equalization accompany the amplitude ripples. At microwave frequencies, modifying the central resonator of

**Figure 1**

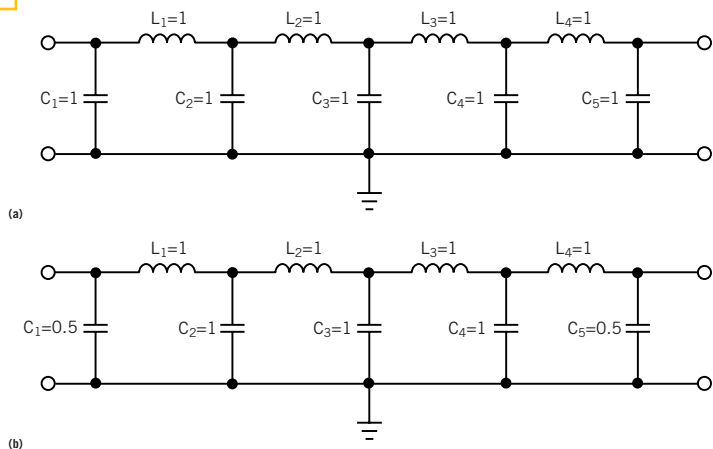

**The equal-element lowpass filter can feature unacceptable passband ripple for some applications (a). A modified filter realizes substantial improvement in passband performance with some reduction in stopband selectivity (b).**

a five-pole bandpass filter leads to improved performance (**Reference 2**).

**Figure 1a** shows the schematic of a nine-pole, equal-element, lowpass-filter prototype. **Figure 1b** shows a comparable schematic of a modified lowpass-filter prototype. By altering the filter input and output capacitors, the modified filter realizes substantial improvement in passband performance with some reduction in stopband selectivity. In the modified equal-element design, all filter inductors are still equal in value, and you need only two capacitor values in a convenient 2-to-1 ratio. **Table 1** shows comparative theoretical amplitude responses for the nine-pole, equal-element lowpass

filter and a nine-pole, modified, equal-element, lowpass filter with inductor-unloaded Qs of 100.

The reference frequency, at normalized frequency  $x=1.0$ , is not the 3-dB cutoff frequency for the filters in **Figure 1**. The 3-dB cutoff frequency occurs close to  $x=1.9$ . This feature differs from Butterworth and Chebyshev filters, for which  $x$  can equal 1.0 at 3-dB cutoff frequencies. You use this normalization for equal-element and modified equal-element designs to calculate the values of the circuit elements.

A nine-pole, modified, equal-element lowpass filter was designed at a reference frequency  $F_R$  of 4.681 MHz, for which

|   |     |
|---|-----|
| Equal-element filter improves passband performance..... | 123 |
| Test batteries without a voltmeter, part 2.....         | 126 |
| SCR phase control yields solid-state switch.....        | 128 |
| Circuit facilitates video fading.....                   | 130 |
| Time-delay relay uses proximity control.....            | 132 |
| Circuit forms shaping amp and amplitude detector.....   | 134 |

**TABLE 1—THEORETICAL AMPLITUDE RESPONSES FOR NINE-POLE, EQUAL-ELEMENT AND MODIFIED, EQUAL-ELEMENT, LOWPASS FILTER**

| Normalized frequency | Frequency (MHz) | Insertion loss of equal-element lowpass filter (dB) | Insertion loss of modified equal-element lowpass filter (dB) |
|----------------------|-----------------|---|--|
| 0                    | 0               | 0.172   | 0.172  |
| 0.1                  | 0.468           | 0.185   | 0.172  |
| 0.2                  | 0.936           | 0.202   | 0.174  |
| 0.3                  | 1.404           | 0.201   | 0.176  |
| 0.4                  | 1.872           | 0.212   | 0.178  |
| 0.5                  | 2.341           | 0.315   | 0.182  |
| 0.6                  | 2.809           | 0.532   | 0.184  |
| 0.7                  | 3.277           | 0.739   | 0.186  |
| 0.8                  | 3.745           | 0.74  | 0.192  |
| 0.9                  | 4.213           | 0.475   | 0.215  |
| 1                    | 4.681           | 0.259   | 0.27   |
| 1.1                  | 5.149           | 0.707   | 0.345  |
| 1.2                  | 5.617           | 1.777   | 0.386  |
| 1.3                  | 6.085           | 2.546   | 0.337  |
| 1.4                  | 6.553           | 2.167   | 0.258  |
| 1.5                  | 7.022           | 0.664   | 0.462  |
| 1.6                  | 7.49            | 1.849   | 1.191  |
| 1.7                  | 7.958           | 5.52  | 1.84   |
| 1.8                  | 8.426           | 5.91  | 1.124  |
| 1.9                  | 8.894           | 3.574   | 2.887  |
| 2                    | 9.362           | 19.255  | 12.533   |
| 2.1                  | 9.83            | 28.937  | 20.678   |
| 2.2                  | 10.298          | 36.285  | 27.288   |
| 2.3                  | 10.766          | 42.426  | 32.953   |
| 2.4                  | 11.234          | 47.794  | 37.977   |
| 2.5                  | 11.703          | 52.612  | 42.53  |
| 2.6                  | 12.171          | 57.011  | 46.715   |
| 2.7                  | 12.639          | 61.075  | 50.604   |

Note: Data is for inductor-unloaded Qs of 100.

$x=1$ . For  $50\Omega$  input and output impedances  $Z_0$ , you calculate the normalizing inductance,  $L_0$ , and normalizing capacitance,  $C_0$ , as follows:

$$L_0 = \frac{Z_0}{2\pi \cdot F_R} = 1.7 \mu\text{H};$$

$$C_0 = \frac{1 \times 10^{-6}}{2\pi \cdot F_R Z_0} = 680 \text{ pF}.$$

You then use these values of  $L_0$  and  $C_0$  to denormalize the filter to actual circuit-element values. Filter inductors  $L_1, L_2, L_3$ , and  $L_4$  are equal to  $L_0 = 1.7 \mu\text{H}$ . Interior filter capacitors  $C_2, C_3$ , and  $C_4$  are equal to  $C_0 = 680 \text{ pF}$ . The filter input and output capacitors,  $C_1$  and  $C_5$ , are equal to

$0.5 \times C_0 = 340 \text{ pF}$ . In the actual filter, the input and output capacitors are standard 330-pF values. The nine-pole, modified, equal-element, lowpass filter was constructed in a die-cast aluminum box with BNCs. The filter circuit was fabricated using vector board. All capacitors were 5%-tolerance polypropylene units. All inductors used 18 turns of number 26 magnet wire on Micro Metals' T37-2 toroids.

Table 2 shows the measured amplitude-response data. The measured data provides reasonable correlation between theory and experiment and shows substantial improvement in amplitude response over most of the filter passband with some degradation in stopband performance.

**TABLE 2—MEASURED AMPLITUDE RESPONSE FOR NINE-POLE, MODIFIED, EQUAL-ELEMENT, LOWPASS FILTER**

| Frequency (MHz) | Insertion loss (dB) |
|-----------------|---------------------|
| 2               | 0.1                 |
| 4               | 0.15                |
| 5               | 0.2                 |
| 5.5             | 0.25                |
| 6               | 0.3                 |
| 6.5             | 0.4                 |
| 7               | 0.6                 |
| 7.25            | 0.85                |
| 7.5             | 1.15                |
| 7.75            | 1.4                 |
| 8               | 1.5                 |
| 8.1             | 1.1                 |
| 8.2             | 0.8                 |
| 8.3             | 1.5                 |
| 8.4             | 1.1                 |
| 8.5             | 0.8                 |
| 8.6             | 1.25                |
| 8.7             | 0.75                |
| 8.8             | 1.25                |
| 8.9             | 2.4                 |
| 9               | 4                   |
| 9.25            | 9.2                 |
| 9.5             | 13.7                |
| 10              | 21.9                |
| 11              | 34.6                |
| 12 to 30        | Greater than 45     |

You can transform the modified, equal-element, lowpass prototype into useful highpass and bandpass filters with similar design features.

REFERENCES

1. Taub, JJ, "Design of Minimum Loss Band-Pass Filters," *Microwave Journal*, Volume 6, pg 67, November 1963.
2. Bawer, R, and G Kefalas, "A Modified Equal-Element Band-Pass Filter," *IRE Trans MTT*, Volume MTT-5, pg 175, July 1957.


Is this the best Design Idea in this issue? Vote at [www.ednmag.com/ednmag/vote.asp](http://www.ednmag.com/ednmag/vote.asp).

# Test batteries without a voltmeter, part 2

Harry Gibbens Jr, PowerStream Technology, Orem, UT

**F**ROM A HIGH-volume-production point of view of the Design Idea “Test batteries without a voltmeter” (EDN, Nov 9, 2000, pg 167), it is a time-consuming and laborious task to tweak the large number of potentiometers on each of the comparator input references. An alternative to this onerous adjustment chore is to replace all potentiometers with 1%-tolerance fixed resistors (Figure 1). Before calculating each voltage-reference resistance value, you should use a reasonable selected total resistance value,  $R_{TOT}$ , ranging from 100 k $\Omega$  to 1 M $\Omega$ . You can usually obtain each of the resistance-divider values from off-the-shelf fixed resistors. After calculating all the resistance-divider values (with  $R_{TOT} = 100$  k $\Omega$ ), if the closest reasonable stock values are unavailable, just increase the value of  $R_{TOT}$ . For the example in Figure 1, you calculate the values using a spreadsheet to obtain quick results.

**Figure 1**

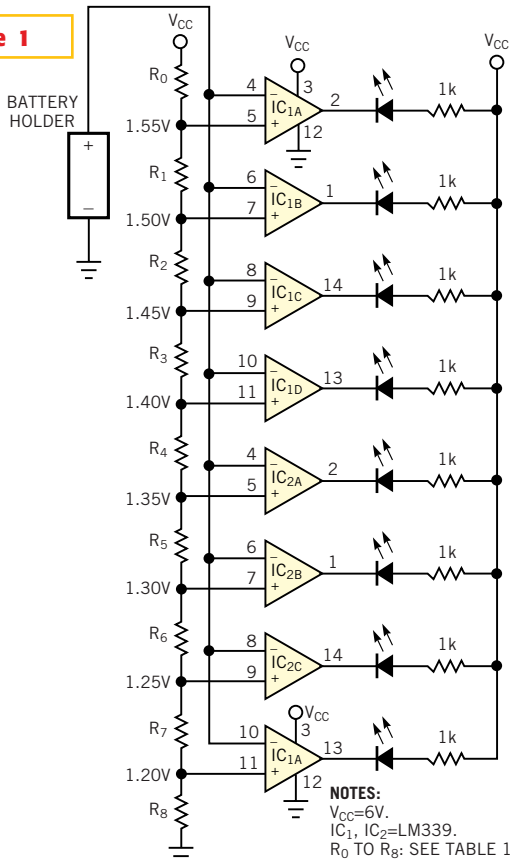

**Fixed, 1%-tolerance resistors eliminate the need to trim potentiometers in this battery-testing circuit.**

This example uses  $R_{TOT} = 182$  k $\Omega$ . All the calculations use Kirchoff’s law:

$$V_X = V_{TOT} \left( \frac{R_X}{R_1 + R_2} \right)$$

Rearranging the terms in the formula, you determine the resistance value,  $R_X$ :

$$R_X = R_{TOT} \left( \frac{V_X}{V_{TOT}} \right)$$

where  $V_X$  is each comparator’s reference voltage,  $V_{REFX}$ ;  $V_{TOT} = V_{CC}$ ; and  $R_{TOT}$  is the

total resistance value. An example follows:

$$\begin{aligned} R_{FORM1} &= 182 \text{ k}\Omega \left( \frac{1.55\text{V}}{6\text{V}} \right) \\ &= 182 \text{ k}\Omega(0.2583) \\ &= 47.01 \text{ k}\Omega. \end{aligned}$$

Next, calculate the first resistance value,  $R_0$ , by using the formula

$$R_X = R_{TOT} - R_{TOT} \left( \frac{V_X}{V_{TOT}} \right) = R_{TOT} - R_{FORMX}$$

$$\begin{aligned} R_0 &= 182 \text{ k}\Omega - 182 \text{ k}\Omega \left( \frac{1.55\text{V}}{6\text{V}} \right) \\ &= 182 \text{ k}\Omega - 182 \text{ k}\Omega(0.2583) \\ &= 182 \text{ k}\Omega - 47.01 \text{ k}\Omega \\ &= 134.99 \text{ k}\Omega. \end{aligned}$$

Calculate the rest of the resistor values,  $R_1$  through  $R_7$ , by using the formula

$$\begin{aligned} R_{X+1} &= R_{TOT} \left( \frac{V_X}{V_{TOT}} \right) - R_{TOT} \left( \frac{V_{X+1}}{V_{TOT}} \right) = \\ &R_{FORMX} - R_{FORMX+1}. \end{aligned}$$

For example, for  $R_1$ :

$$\begin{aligned} R_1 &= 100 \text{ k}\Omega \left( \frac{1.55\text{V}}{6\text{V}} \right) - 100 \text{ k}\Omega \left( \frac{1.5\text{V}}{6\text{V}} \right) \\ &= 1.51 \text{ k}\Omega. \end{aligned}$$

Finally, use the rearranged formula to

manually selected value. The first step is to calculate the “Formulated R” in Table

**TABLE 1—CALCULATED VALUES FOR BATTERY TESTER**

| Reference voltage | Voltage (V) |      | Formulated R k $\Omega$ | Calculated R k $\Omega$ | Fixed R k $\Omega$ |
|-------------------|-------------|------|-------------------------|-------------------------|--------------------|
| $V_{TOT}$         | 6           |      | $R_{TOT}$               | 182                     |                    |
| $V_{REF1}$        | 1.55        | 0.26 | 47.01                   | $R_0$                   | 134.99             |
| $V_{REF2}$        | 1.5         | 0.25 | 45.5                    | $R_1$                   | 1.51               |
| $V_{REF3}$        | 1.45        | 0.24 | 43.99                   | $R_2$                   | 1.51               |
| $V_{REF4}$        | 1.4         | 0.23 | 42.46                   | $R_3$                   | 1.53               |
| $V_{REF5}$        | 1.35        | 0.23 | 40.95                   | $R_4$                   | 1.51               |
| $V_{REF6}$        | 1.3         | 0.22 | 39.44                   | $R_5$                   | 1.51               |
| $V_{REF7}$        | 1.25        | 0.21 | 37.91                   | $R_6$                   | 1.53               |
| $V_{REF8}$        | 1.2         | 0.2  | 36.4                    | $R_7$                   | 1.5                |
|                   |             |      |                         | $R_8$                   | 36.4               |

find the last resistance value,  $R_8$ .

$$R_8 = 182 \text{ k}\Omega \left( \frac{1.2\text{V}}{6\text{V}} \right) = R_{\text{FORM}8} \\ = 36.4 \text{ k}\Omega.$$

In **Table 1**, you match the rounded-off

calculated resistance value (Calculated R) to the nearest available fixed-resistor value (Fixed R) as shown in the last two columns. Note that  $R_0$  consists of two series-connected resistors. You can download the table of 1%-tolerance resistor values from EDN's Web site, www.edn

mag.com. Click on "Search Databases" and then enter the Software Center to download the .gif file for Design Idea #2654.

**Is this the best Design Idea in this issue?** Vote at [www.ednmag.com/ednmag/vote.asp](http://www.ednmag.com/ednmag/vote.asp).

## SCR phase control yields solid-state switch

James Keith, York, PA

**S**CRs (SILICON-CONTROLLED rectifiers), or thyristors, have higher current and voltage ratings, lower conduction losses, and more robustness than triacs. For these reasons, SCRs are better suited to high-power applications. For example, you can use two SCRs to configure a 100 or 200A, 460V control circuit. **Table 1** lists some of the advantages of SCRs over triacs. The main challenge is driving the SCRs: You now have two gates, rather than one, to drive. Furthermore, the gates are referenced to opposite polarities with a significant voltage difference. The circuit in **Figure 1** solves the problem with two PUTs (programmable unijunction transistors), one connected to each SCR. Performance is good because the circuit does not "fold back" as inexpensive triac phase controls (dimmers) do. The PUT fires when the timing-capacitor voltage exceeds the PUT reference voltage by one diode drop and dumps the capacitor's charge into the SCR gate.


You adjust the phase delay by varying the charge rate of the capacitor via the potentiometer. You can enhance the balance by matching both the zener-diode voltages and the values of the charging capacitance. You

can obtain 230V operation by using 1.5- to 2- $\mu\text{F}$  timing capacitors. You can achieve 460V-ac operation by using 1200V SCRs; 3- $\mu\text{F}$  timing capacitors; and

a 100-k $\Omega$ , 25W potentiometer. Using the circuit as a solid-state switch is practical; simply replace the voltage-adjust block in the broken lines in **Figure 1** with a *photomod*. A photomod is a unique type of photocoupler that has an LED or incandescent-light source and a cadmium-sulphide photocell. Unique properties of these photocells are their high dark resistance and high voltage ratings.

**Is this the best Design Idea in this issue?** Vote at [www.ednmag.com/ednmag/vote.asp](http://www.ednmag.com/ednmag/vote.asp).

**Figure 1**

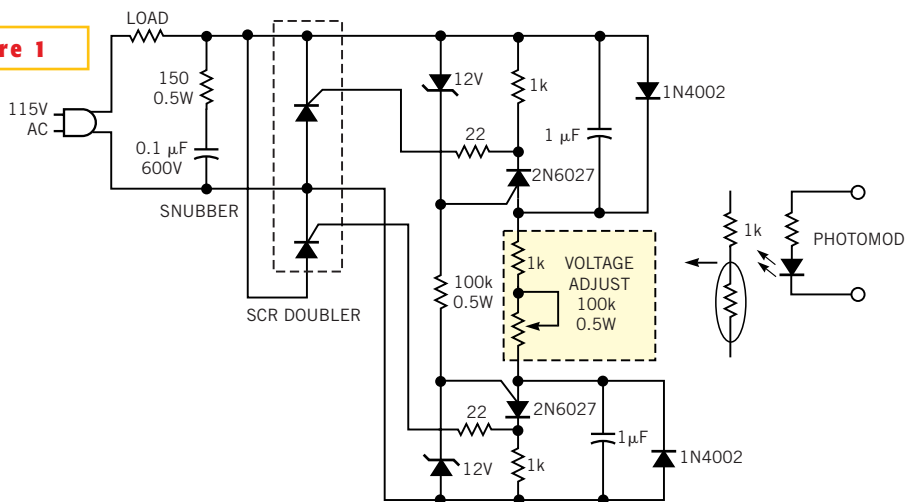

**This SCR phase-control circuit uses one potentiometer and no pulse transformers.**

**TABLE 1—SCR-VERSUS-TRIAC COMPARISON**

| Device                  | SCR                      | Triac        |
|-------------------------|--------------------------|--------------|
| Current rating          | >>50A                    | <40A         |
| Conduction voltage drop | ~1V                      | ~1.5V        |
| Junction temperature    | 125°C                    | 115°C        |
| Thermal resistance      | Low                      | Medium       |
| Maxium voltage          | 1400V                    | 600V         |
| Surge current           | High                     | Limited      |
| Robustness              | High                     | Low          |
| Package                 | Doubler or "hockey puck" | 1/4-in. stud |
| Isolation               | Isolated                 | Nonisolated  |
| Number required         | Two                      | One          |

# Circuit facilitates video fading


*JM Terrade, Clermont-Ferrand, France*

**W**HEN YOU'RE COPYING videotapes, it's sometimes desirable to suppress some passages. Using the pause control of the recorder does not yield satisfactory results. Another method produces better results (Figure 1). The video source connects to the video-in plug, and the recorder connects to the video-out plug. Turning potentiometer  $P_1$  adjusts the image brightness from normal video to a black image. With the  $P_2$  potentiometer ganged to  $P_1$ , the sound also varies accordingly. The objectives in building this circuit are to use inexpensive, readily available components and to obtain batteryless operation. The video signal follows two paths (Figure 2). In the first path, the signal undergoes amplification by a factor of two and connects to one end of a poten-

tiometer. In the second path, the synchronization pulse, separated from the input signal, connects to the other end of the potentiometer. The wiper of the potentiometer connects to the second video

amplifier, which provides the video output.


When you adjust  $P_1$ 's wiper from one end to the other, the video image disappears and fades to a black screen. Because  $P_1$  and  $P_2$  are ganged, the sound follows the image brightness. The circuit could have used triple integrated video amplifiers, such as an AD813, and a video sync separator, such as an LM1881. However, these ICs are expensive (approximately \$25) compared with the six standard transistors shown in Figure 2.  $R_1$  sets the input impedance at  $75\Omega$ .  $Q_1$ ,  $Q_2$ , and associated components form a video amplifier with an approximate gain of two.  $R_2$ ,  $R_3$ , and  $D_1$  set the dc voltage, and  $C_1$  blocks any dc voltage from the source. The amplified video signal connects

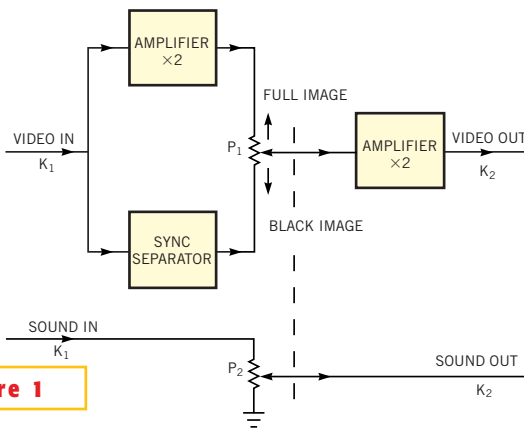

**Figure 1**

**A simple circuit provides for effective video and audio fading when you're recording source material.**

**Figure 2**

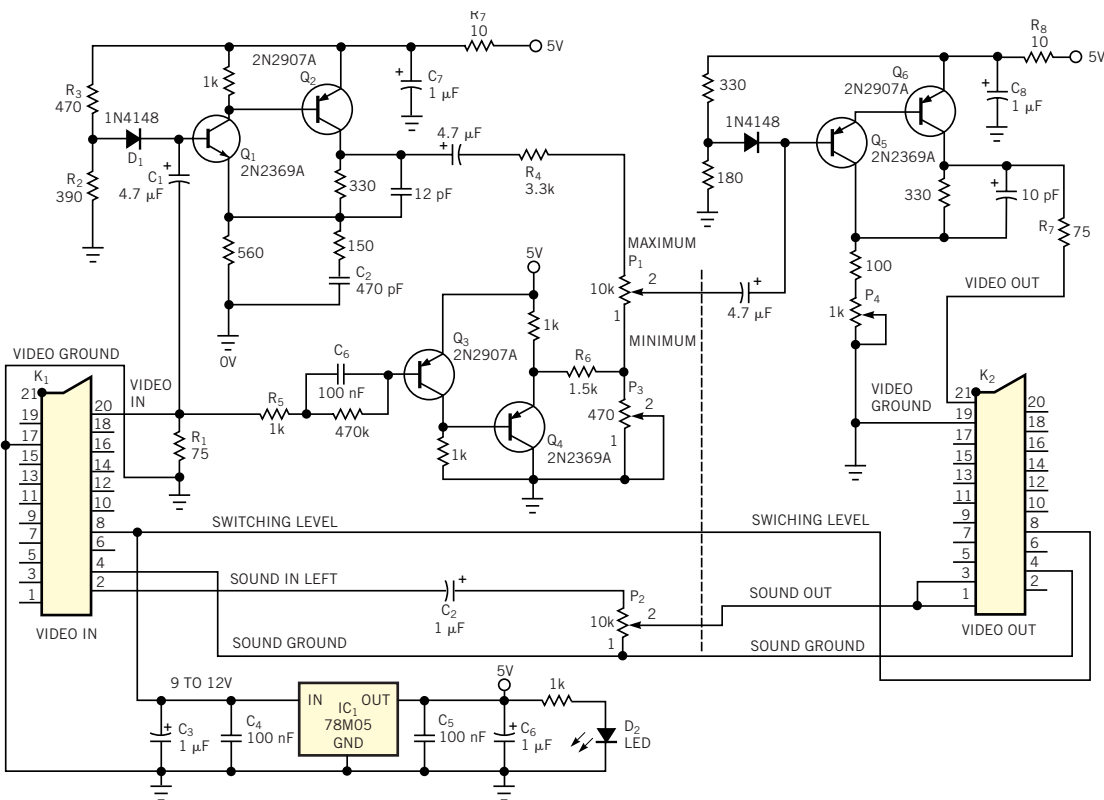

**A handful of transistors and associated components yields a professional-quality video fader.**

to  $P_1$  through  $R_4$  and the  $C_1$  dc-blocking capacitor.  $R_5$ ,  $Q_3$ ,  $Q_4$ , and associated components form a sync separator. The sync pulse connects to the bottom of  $P_1$  through  $R_6$  and  $P_3$ , an adjustable voltage divider. The wiper of  $P_1$  connects to the second video amplifier comprising  $Q_5$ ,  $Q_6$ , and associated components. You can adjust the amplification with  $P_4$ .  $R_7$  sets the output impedance at  $75\Omega$ .

$P_2$ , ganged to  $P_1$ , is a simple voltage divider, using  $C_2$  to block dc voltages. The sound input uses the left channel, and the

output goes to both the left and right channels. With a video source connected to video in, a dc voltage of 9 to 12V appears at Pin 8 of the video plug.  $IC_1$  and the  $C_2$  through  $C_6$  capacitors derive power from this pin and provide a stable 5V for the circuit.  $D_2$  is a high-brightness LED that indicates that a video source is present.  $R_7$ ,  $C_7$ ,  $R_8$ , and  $C_8$  provide decoupled supplies for the amplifiers. Video cables are often of poor quality. For that reason, the circuit in **Figure 2** provides for amplification of the video signal. Also,

compensation of the first amplifier provides amplification of color burst with a concomitant improvement of video quality. To adjust the circuit, first turn  $P_1$  fully clockwise and then adjust  $P_4$  for a good video image. Then, turn  $P_1$  fully counterclockwise and adjust  $P_3$  to obtain a stable black image.

**Is this the best Design Idea in this issue?** Vote at [www.ednmag.com/ednmag/vote.asp](http://www.ednmag.com/ednmag/vote.asp).

## Time-delay relay uses proximity control

Dennis Eichenberg, Parma Heights, OH

**Y**OU CAN BUILD A CIRCUIT that allows a passerby to briefly operate model trains in a display window (**Figure 1**). The design uses a proximity detector rather than a pushbutton switch to eliminate the need to mount and wire any equipment outdoors. The circuit worked well in this application and other applications. The heart of the circuit is the quad CMOS NAND gate,  $IC_1$ . A human hand near the sensor induces 60-Hz power-line noise into  $IC_{1A}$ , and this IC triggers  $IC_2$ .  $IC_2$  is configured as a monostable multivibrator, with a period equal


to  $1.1(R_3+R_4)(C_3)$ . The period is adjustable from approximately 0.5 to 50 sec. The sensitivity of the circuit depends on the size of the sensor. A 10-in.-sq piece of screen mounted inside the display window works well for this application, because it permits complete visibility through the sensor. The circuit triggers several inches away from the window in this application.

You can manually or automatically operate the circuit through the single-pole, double-throw, center-off switch,  $S_1$ . In automatic operation, receptacle  $J_1$  is ac-

tive when  $IC_2$  drives relay  $K_1$  on. Lamp  $LP_1$  indicates when the load is active. Lamp  $LP_2$  indicates when the circuit is in automatic mode.  $J_1$  is active whenever  $S_1$  is in the on position, as  $LP_1$  indicates.  $V_{CC}$  for the circuit comes from transformer  $T_1$ , rectifier  $D_1$ , and filter capacitors  $C_1$  and  $C_2$ . The load rating for the circuit depends on the selection of fuse  $F_1$ , switch  $S_1$ , relay  $K_1$ , and receptacle  $J_1$ .

**Is this the best Design Idea in this issue?** Vote at [www.ednmag.com/ednmag/vote.asp](http://www.ednmag.com/ednmag/vote.asp).

**Figure 1**

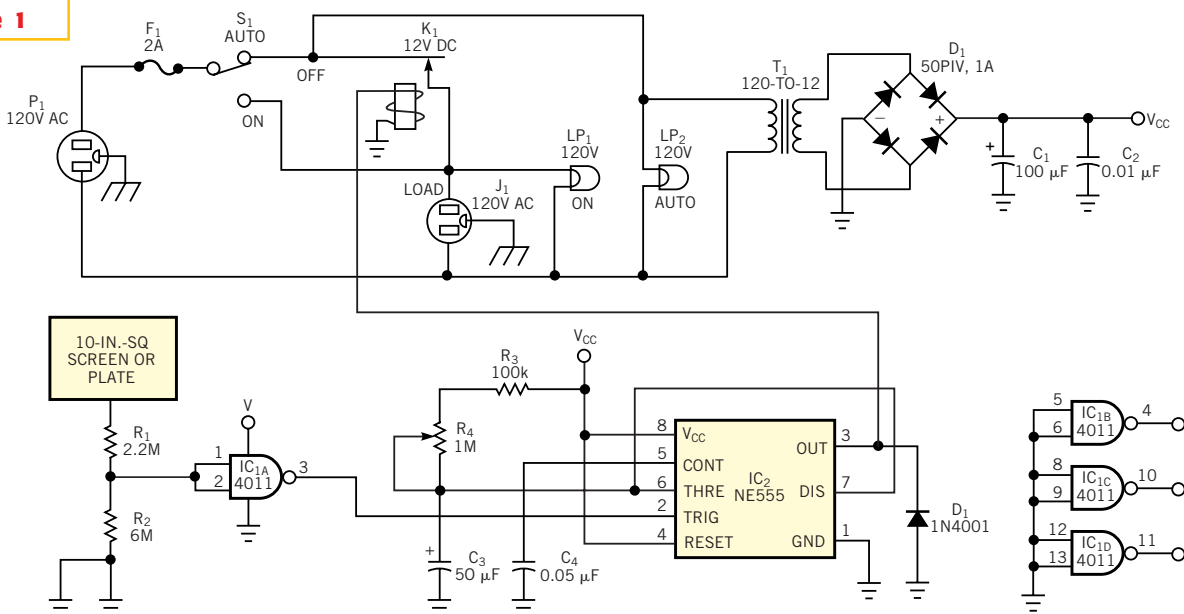


**A proximity sensor turns a load on when a human hand comes near the sensor screen.**

# Circuit forms shaping amp and amplitude detector

Elio Rossi, ITESRE-CNR, Bologna, Italy


**T**HE USE OF SOLID-STATE detectors connected to charge amplifiers requires appropriate conditioning of the output signals, because of the signals' long decay time. Moreover, you must "stretch" the peaks of the shaped pulses for a period sufficient for A/D conversion. For a single detector, you can use a relatively expensive module. For a large detector array, you need to develop an ASIC. For a moderate number of detectors, you can use an inexpensive circuit that handles an array of 19 drift diodes connected to a scintillating crystal of cesium-iodide (Figure 1). The two ICs, an OP37 and an AD823, provide the correct gain and the semi-gaussian conditioning of the input pulses. The conditioning involves a differentiating input with pole-zero adjust in the gain-of-35 first stage, a lowpass Sallen-

**Figure 2**

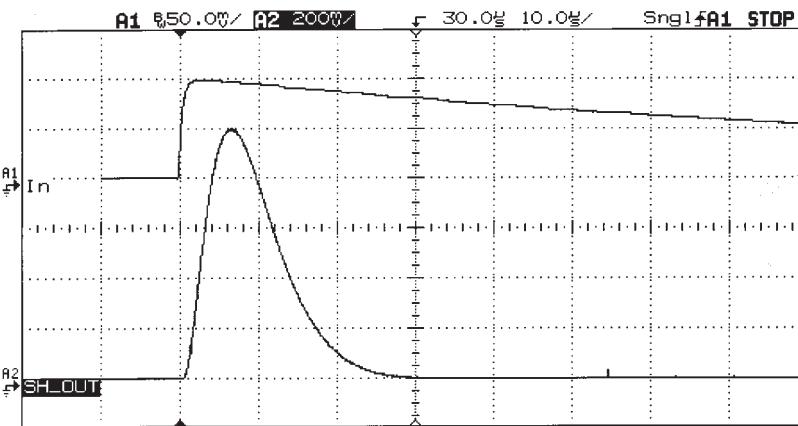

At the AD823 output in Figure 1, the signal peaks in 6 msec. A peak detector then "stretches" the signal.

**Figure 1**

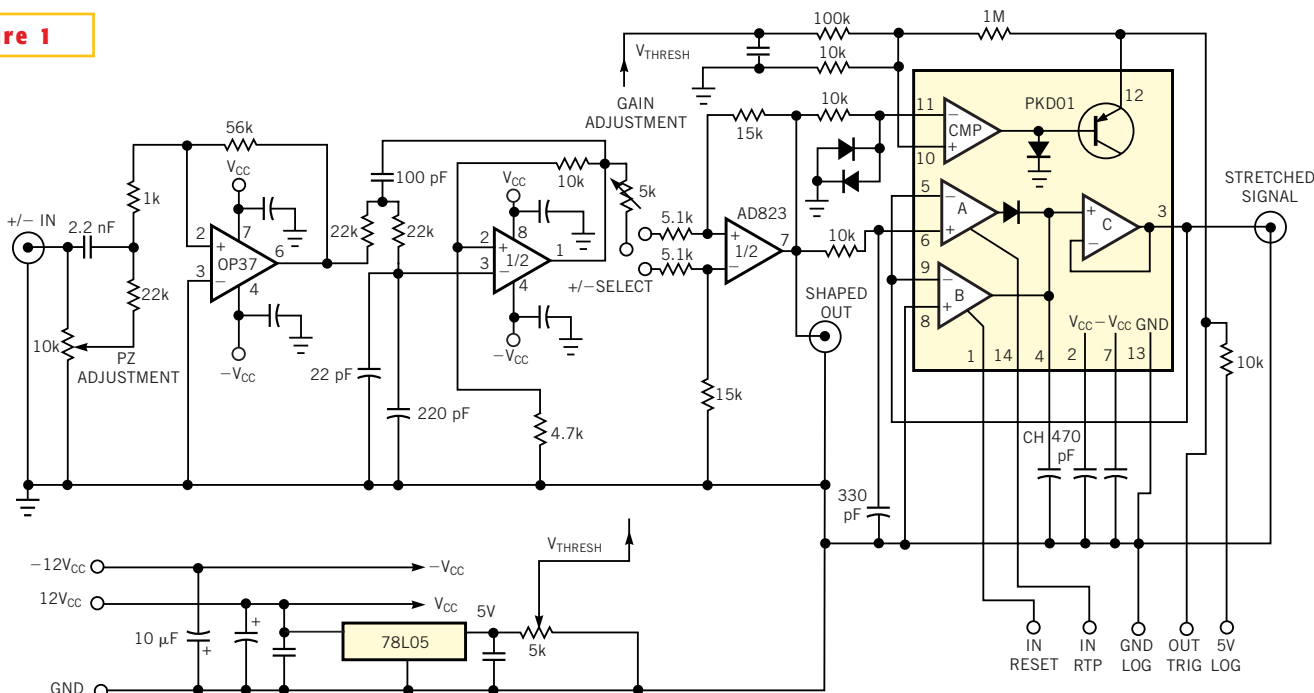


A few linear ICs form the basis of a shaping amplifier and peak-amplitude detector.

Key filter in the unity-gain second stage, and a gain-adjustable third stage.

**Figure 2** shows a peaking time of 6  $\mu$ sec with a gain of 50 to 100V/V. The circuit can use either a positive or a negative input signal.

The third IC, a PKD01, acts as a “stretcher” circuit with a built-in trigger discriminator. To measure the performance of the circuit, the design uses four external one-shot multivibrators, a precision pulse generator, and a multichannel analyzer in sample mode. The discriminator output triggers the sequence of the one-shots, which in turn open the in reset and close the in rise-time-protection, gated amplifiers, A and B (figures 1 and 3). This action allows the hold capacitor to reach the peak of the integrated (via the 10-k $\Omega$ , 330-pF network) input pulse, so that an A/D converter can begin its conversion. The circuit must maintain the stretched signal via the reset pulse until the end of conversion. Input integration is necessary to generate a delay between the aperture of the reset

**Figure 3**

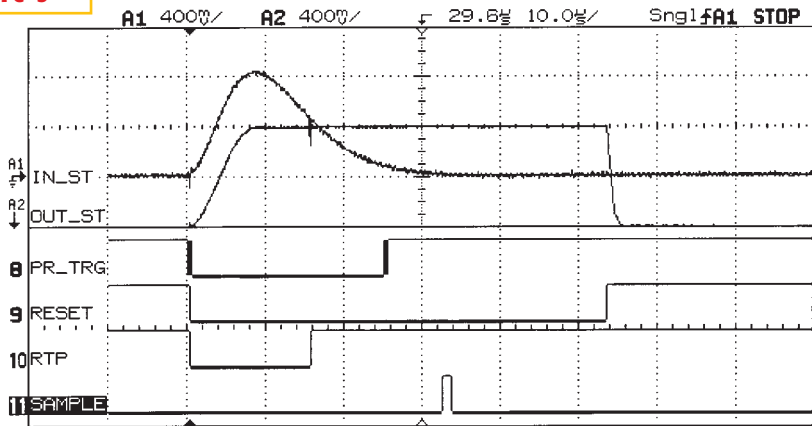

**In the second waveform down, the peak detector provides a sample/hold function and preserves the peak value of the signal.**

command and the peak of the input pulses to maintain the linearity of the low-level signal. Also, the approximately 0.7V/ $\mu$ sec slew rate of the stretched output requires at least 8  $\mu$ sec in the peak-

ing time of the input signal to obtain a stretched signal output greater than 5V.

**Is this the best Design Idea in this issue?** Vote at [www.ednmag.com/ednmag/vote.asp](http://www.ednmag.com/ednmag/vote.asp).