

# **A Users Guide to COPS™ Oscillator Operation**

National Semiconductor  
Application Note 326  
Jim Murashige  
April 1983



**A Users Guide to COPS Oscillator Operation**

**AN-326**

The Colpitts configuration is commonly shown in microprocessor oscillator circuits (*Figure 5*) with the inductive X3 replaced by a crystal for reasons we shall soon see. The equivalent electrical model of a crystal is shown in *Figure 4b* and a plot of its Reactance versus Frequency shown in *Figure 4c*. R-L-C represent the electro-mechanical properties of the crystal and  $C_0$  the electrode capacitance. There are 2 important points on the reactance curve labeled  $f_a$  and  $f_b$ .

$$\text{At } f_a = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

the crystal is at series resonance with L and C canceling each other out leaving only a nonreactive R for 0 phase shift. This mode of operation is important in oscillator circuits where a non-inverting amplifier is used and 0° phase shift must be preserved.

$$\text{At } f_b = \frac{1}{2\pi} \sqrt{\frac{1}{LC} + \frac{1}{LC_0}}$$


which is just a little higher than  $f_a$  the crystal is at parallel resonance and appears very inductive or capacitive. Note that the crystal will only appear inductive between  $f_a$  and  $f_b$  and that it becomes highly inductive very quickly. In addition  $f_b$  is only a fraction of a percent higher than  $f_a$ . Therefore the only time that the crystal will satisfy the  $X_3 = -(X_1 + X_2)$  condition in the Colpitts configuration of *Figure 5* is when the circuit is oscillating between  $f_a$  and  $f_b$ . The exact frequency will be the one which gives an inductive reactance large enough to cancel out:

$$X_1 + X_2 = \frac{1}{\omega C_1} + \frac{1}{\omega C_2} = \frac{1}{\omega} \left[ \frac{1}{C_1} + \frac{1}{C_2} \right] = \frac{1}{2\pi f} \left[ \frac{1}{C_L} \right]$$

Therefore by varying  $C_1$  or  $C_2$  we can trim slightly the oscillator frequency.


**a. Circuit Symbol**

TL/DD/5139-4

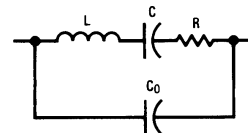


**b. Electrical Equivalent**

TL/DD/5139-5

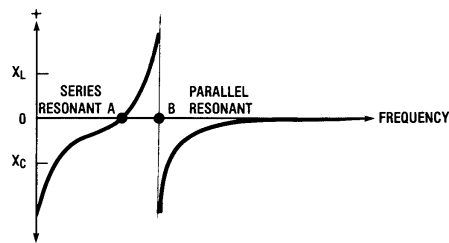

TL/DD/5139-6

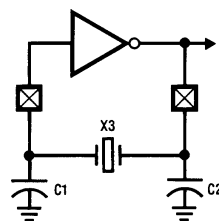**c. Reactance Versus Frequency**  
**FIGURE 4. Quartz Crystal**



TL/DD/5139-7

**FIGURE 5. Colpitts Oscillator**

The Q of a circuit is often bounced around in comparing different circuits and can be viewed graphically here as the slope of the reactance curve between  $f_a$  and  $f_b$ . Obviously the steeper the curve the smaller the variation in  $f$  necessary to restore the Barkhausen Phase Shift Criterion. In addition a lower Q (more R) means that the reactance curve won't peak as high at  $f_b$ , necessitating a smaller  $X1 + X2$ . When selecting crystals the user should be aware that the frequency stamped on the cans are for either parallel or series resonance, which, although very close, may matter significantly in the particular application.

An actual MOS circuit implementation of *Figure 5* is shown in *Figure 6*. It consists of a MOS inverter with depletion load and the crystal  $\pi$  network just presented. External to the COPS chips are the  $R_f$  and  $R_g$  resistors.  $R_f$  provides bias to the MOS inverter gate  $V_g = V_o$ . Since the gate draws no current  $R_f$  can be very large ( $M\Omega$ ) and should be, since we do not wish it to interact with the crystal network.  $R_g$  increases the output resistance of the inverter and keeps the crystal from being over driven.

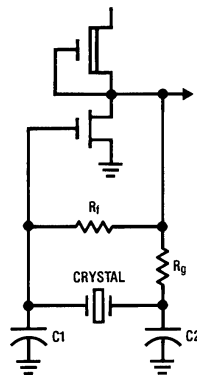


FIGURE 6. MOS Oscillator

TL/DD/5139-8

Of course the feedback network doesn't have to have the configuration of *Figure 3* and can be anything so long as the Barkhausen Phase Shift Criterion is satisfied. One popular configuration is shown in *Figure 7* where the phase shift will be  $180^\circ$

$$\text{at } f = \frac{1}{(2\pi RC\sqrt{6})}$$


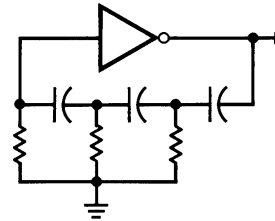


FIGURE 7. R-C Phase Shift Oscillator

TL/DD/5139-9

## REFERENCES

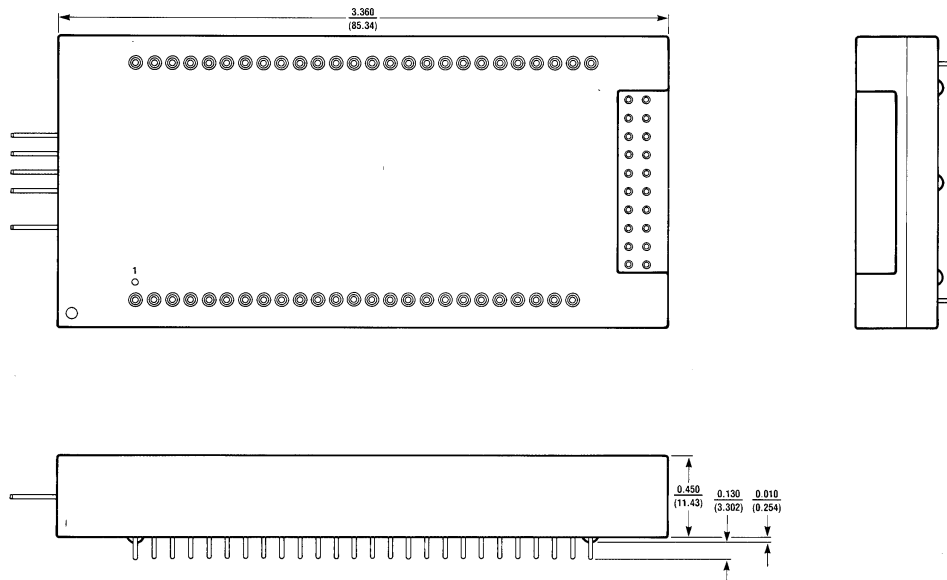1. Crystal/INS8048 Oscillator, AN-296, March 1982, National Semiconductor
2. Oscillator Characteristics of COPS Microcontrollers, CN-5, Feb. 1981, National Semiconductor
3. Integrated Electronics, Chapter 14, Millman and Halkias 1972
4. Handbook of Electronics Calculations, Chapter 9, Kaufman and Seidman 1979
5. 1982 COPS Microcontroller Databook, National Semiconductor



TL/DD/5139-10

## LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



**National Semiconductor Corporation**  
1111 West Bardin Road  
Arlington, TX 76017  
Tel: 1(800) 272-9959  
Fax: 1(800) 737-7018

**National Semiconductor Europe**  
Fax: (+49) 0-180-530 85 86  
Email: cnjwge@tevm2.nsc.com  
Deutsch Tel: (+49) 0-180-530 85 85  
English Tel: (+49) 0-180-532 78 32  
Français Tel: (+49) 0-180-532 93 58  
Italiano Tel: (+49) 0-180-534 16 80

**National Semiconductor Hong Kong Ltd.**  
19th Floor, Straight Block,  
Ocean Centre, 5 Canton Rd.  
Tsimshatsui, Kowloon  
Hong Kong  
Tel: (852) 2737-1600  
Fax: (852) 2736-9960

**National Semiconductor Japan Ltd.**  
Tel: 81-043-299-2309  
Fax: 81-043-299-2408