

INDEX

- Air gap
 - in coupled inductor, 502
 - in flyback transformer, 503
 - in inductor, 464-466, 498, 505, 509
 - in transformer, 469
- A_L (mH/1000 turns), 509
- American wire gauge (AWG)
 - data, 755-756
 - design examples, 527, 531
- Amorphous alloys, 473
- Ampere's law, 457-458
- Amp-second balance (*see* Capacitor charge balance)
- Apparent power, 550
- Artificial ramp
 - circuit, 415
 - effect on CPM boost low-harmonic rectifier, 637-639
 - effect on line-to-output transfer function of CCM buck, 437-438
 - effect on small-signal CCM models, 428-438
 - effect on small-signal DCM models, 438-447
 - effect on stability of CPM controllers, 414-418
- Asymptotes (*see* Bode plots)
- Audiosusceptibility $G_{v_o}(s)$ (*see* Line-to-output transfer function)
- Average current control
 - feedforward, 635-636
 - in low-harmonic rectifier systems, 593-598, 634-636, 649, 650-652
 - modeling of, 649-652
- Averaged switch modeling, 239-245, 390-403
 - of current-programmed CCM converters, 423-428
 - of current-programmed DCM converters, 438-447
 - in discontinuous conduction mode, 370-390
 - equivalent circuit modeling of switching loss, 241-245
 - examples
 - nonideal buck converter, 241-245
 - DCM buck converter, 393-400
 - CCM SEPIC, 757-762
 - generalization of, 390-403
 - of ideal CCM switch networks, 242, 377, 757-762
 - of ideal DCM switch networks, 377
 - of quasi-resonant converters, 732-737
- Average power
 - and Fourier series, 542-543
 - modeled by power source element, 375-379, 423-428, 438-447
 - in nonsinusoidal systems, 542-555
 - predicted by averaged models, 57
 - power factor, 546-550
 - sinusoidal phasor diagram, 550-551
- Averaging
 - approximation, discussion of, 195-196, 200-202
 - averaged switch modeling, 239-245
 - basic approach, 198-209

- capacitor charge balance, 24
- circuit, 231-245
- to find dc component, 6, 16
- flyback ac model, 209-218
- inductor volt-second balance, 22-23
- introduction to, 193-198
- modeling efficiency and loss via, 57
- to model rectifier output, 645-647
- to model 3 ϕ converters, 611-614
- of quasi-resonant converters
 - ac modeling, 732-737
 - dc analysis, 712-728
- state-space, 218-231
- Battery charger, 9, 70
- B-H* loop
 - in an ac inductor, 499-500
 - in a conventional transformer, 153, 500-501
 - in a coupled inductor, 501-502
 - in a filter inductor, 497-499
 - in a flyback transformer, 502-503
 - modeling of, 458-460
- Bidirectional dc-dc converters, 70
- Bipolar junction transistor (BJT)
 - breakdown mechanisms in, 86-87
 - construction and operation of, 82-87
 - current crowding, 85-86
 - Darlington-connected, 87
 - idealized switch characteristics, 65-66
 - on resistance, 53, 82
 - quasi-saturation, 82-83, 86
 - storage time, 84
 - stored minority charge in, 82-86
 - switching waveforms, 83-86
- Bode plots (*see also* Harmonic trap filters, sinusoidal approximation)
 - asymptote analytical equations, 275-276
 - CCM buck-boost example, 289-292
 - combinations, 272-276
 - complex poles, 276-282
 - frequency inversion, 271-272
 - graphical construction of, 296-309
 - addition, 296-301
 - closed-loop transfer functions, 329-332
 - division, 307-309
 - parallel combination, 301-307
 - parallel resonance, 301-303
 - series resonance, 298-303
 - impedance graph paper, 307
 - nonminimum phase zero, 269-271
 - reactance graph paper, 307
 - real pole, 263-268
 - real zero, 268-269
 - RHP zero, 269-271
 - transfer functions of buck, boost, buck-boost, 292-293
- Body diode (*see* MOSFET)

- Boost converter (*see also* Bridge configuration, Push-pull isolated converters)
 - active switch utilization in, 179, 608
 - averaged switch model, DCM, 380-381
 - circuit-averaged model, 233-239
 - current-programmed
 - averaged switch model, CCM, 424-425
 - averaged switch model, DCM, 443-444
 - small-signal ac model, CCM, 427-428, 430-431
 - small-signal ac model, DCM, 445-447
 - as inverted buck converter, 136-137
 - as low-harmonic rectifier, 594-597, 605-609, 617, 627-634
 - nonideal analysis of, 43-51, 53-57
 - quasi-resonant ZCS, 722-723
 - small-signal ac model
 - CCM, 208-210, 251
 - DCM, 385-390
 - steady-state analysis of,
 - CCM, 24-29
 - DCM, 121-125
 - transfer functions, CCM, 292-293
- Bridge configuration (dc-dc converters)
 - boost-derived full bridge, 171-172
 - buck-derived full bridge, 154-157
 - buck-derived half bridge, 157-159
 - full bridge transformer design example, 528-531
 - minimization of transformer copper loss in, 516-517
- Bridge configuration (inverters)
 - single phase, 7-8, 142-145, 148-150
 - three phase, 70, 143-148
- Buck-boost converter (*see also* Flyback converter)
 - 3 ϕ ac-dc rectifier, 615-616, 619
 - averaged switch model, DCM, 370-381
 - as cascaded buck and boost converters, 138-141
 - current-programmed
 - averaged switch model, DCM, 438-444
 - more accurate model, CCM, 430-432
 - simple model, CCM, 419-423
 - small-signal ac model, DCM, 445-447
 - dc-3 ϕ ac inverter, 71-72, 615-616
 - DCM characteristics, 115, 127-129, 381
 - as low-harmonic rectifier, 598-599
 - manipulation of ac model into canonical form, 248-251
 - nonideal, state-space averaged model of, 227-232
 - noninverting version, 139, 148-149
 - as rotated three-terminal cell, 141-142
 - small-signal ac model, CCM, 208-210, 251
 - small-signal ac model, DCM, 382-388
 - transfer functions, CCM, 289-293
 - transformer isolation in, 166-171
- Buck converter (*see also* Bridge configuration, Forward converter, Push-pull isolated converters), 6, 15-23, 34-35
 - active switch utilization in, 179
 - averaged switch model, 239-245
 - current-programmed

- averaged switch model, CCM, 423-427
 - averaged switch model, DCM, 442-447
 - small-signal ac model, CCM, 421-427, 431-438
 - small-signal ac model, DCM, 442-447
 - equivalent circuit modeling of,
 - small-signal ac, CCM, 208-210, 251
 - small-signal ac, DCM, 385-388, 393-400
 - steady-state, CCM, 51-53
 - steady-state, DCM, 380-381
 - as high power factor rectifier
 - single phase, 599
 - three phase, 614-615
 - multi-resonant realization, 729
 - quasi-square-wave resonant realizations, 730-731
 - quasi-resonant realizations
 - ac modeling of, 732-737
 - zero current switching, 662-663, 712-722, 723-724
 - zero voltage switching, 728
 - small-signal ac model
 - CCM, 208-210, 251
 - DCM, 385-390
 - steady-state analysis of,
 - CCM, 17-22, 23, 34-35, 51-53
 - DCM, 111-121, 380-381
 - switching loss in, 94-101, 241-245
 - employing synchronous rectifier, 73-74
 - transfer functions, CCM, 292-293
- Buck² converter, 149, 151
- Buck 3 ϕ inverter (*see* Voltage source inverter)
- Canonical circuit model, 245-251
 - via generalized switch averaging, 402-403
 - manipulation into canonical form, 248-251
 - parameters for buck, boost, buck-boost, 251
 - physical development of, 245-248
 - transfer functions predicted by, 247-248, 292-293
- Capacitor amp-second balance (*see* Capacitor charge balance)
- Capacitor charge balance
 - boost converter example, 27
 - Cuk converter example, 31-32
 - definition, 24
 - in discontinuous conduction mode, 115
 - nonideal boost converter examples, 45, 55
- Capacitor voltage ripple
 - boost converter example, 28-29
 - buck converter example, 34-35
 - in converters containing two-pole filters, 34-35
 - Cuk converter example, 32-34
- Cascade connection of converters, 138-141
- Characteristic value α (current programmed mode), 414, 417-418, 435-436
- Charge balance (*see* Capacitor charge balance)
- Circuit averaging (*see also* Averaged switch modeling), 231-245
 - averaging step, 235
 - boost converter example, 233-238

- linearization, 235-238
- obtaining a time-invariant network, 234-235
- summary of, 231-233
- Commutation
 - failure, 574
 - notching, 575
 - in 3 ϕ phase controlled rectifier, 573-575
- Compensators (*see also* Control system design)
 - design example, 346-354
 - lag, 343-345
 - lead, 340-340, 350-351
 - PD, 340-343, 350-351
 - PI, 343-345
 - PID, 345-346, 352-354
- Complex power, 550-551
- Computer power supply, 8-9
- Computer spreadsheet, design using, 180-183
- Conduction loss (*see* Copper loss, Semiconductor conduction loss)
- Conductivity modulation, 75, 79, 82, 87, 90
- Control system design (*see also* Compensators, Negative feedback), 323-368
 - compensation, 340-346
 - construction of closed-loop transfer functions, 326-332
 - design example, 346-354
 - for low-harmonic rectifiers
 - approaches, 634-652
 - modeling, 645-652
 - phase margin
 - test, 333-334
 - vs. closed-loop damping factor, 334-338
 - stability, 332-339
 - voltage regulator
 - block diagram, 324-325, 328, 347-349
 - design specifications, 339-340
- Control-to-output transfer function
 - as predicted by canonical model, 248
 - of CCM buck, boost, and buck-boost converters, 292-293
 - of current programmed converters, 422, 427-428, 434-437, 446
 - of DCM converters, 387-390, 396-399
 - of quasi-resonant converters, 733, 736
- Conversion ratio M (*see also* Switch conversion ratio μ)
 - of boost, 18, 26, 127, 381
 - of buck, 18, 120, 381
 - of buck-boost, 18, 128, 381
 - of Cuk converter, 32, 381
 - of loss-free resistor networks, 376-381
 - in low-harmonic rectifiers, 593-595
 - modeling of, 40-43
 - of quasi-resonant converters, 711, 720-723
 - of parallel resonant converter, 676-678, 686-689
 - of SEPIC, 151, 381
 - of series resonant converter, 671-674, 679-686
 - via sinusoidal approximation, 670
- Copper loss

- allocation of window area to minimize, 513-517, 519
- high frequency effects
 - skin effect, 475-476
 - proximity effect, 476-490
- inductor design to meet specified, 503-509
- low frequency, 474
- modeling in converters, 43-53
- Core loss, 471-474, 518
- Coupled inductors
 - in Cuk converter, 494-495, 501
 - in multiple-output buck-derived converters, 501-502, 511
- Crossover frequency, 330-334
- Cuk converter
 - 3ϕ ac-dc converter, 615-616
 - active switch utilization of, 179
 - as cascaded boost and buck converters, 141
 - conversion ratio $M(D)$, 32, 381
 - DCM averaged switch model of, 379-381
 - as low-harmonic rectifier, 597-599, 608
 - as rotated three-terminal cell, 141-142
 - steady-state analysis of, 29-34
 - transformer design example, 524-528
 - with transformer isolation, 176-177
- Current-fed bridge, 148, 150
- Current injection, 359-360
- Current programmed control, 408-451
 - ac modeling of
 - via averaged switch modeling, CCM, 423-428
 - via averaged switch modeling, DCM, 438-447
 - CCM more accurate model, 428-438
 - CCM simple approximation, 418-428
 - artificial ramp, 414-418
 - controller circuit, 409, 415
 - controller small-signal block diagram, 428-432
 - in half-bridge buck converters, 159, 410
 - in low harmonic rectifiers, 636-639
 - oscillation for $D > 0.5$, 411-418
 - in push-pull buck converters, 166, 410
- Current ripple (*see* inductor current ripple)
- Current sense circuit, isolated, 187-188
- Current source inverter (CSI), 146, 148
- Cycloconverter, 1, 72
- Damping factor ζ (*see also* Q -factor), 277
- Dc conversion ratio (*see* Conversion ratio M)
- Dc link, 10
- Dc transformer model
 - in averaged switch models, 237-244, 760-762
 - in canonical model, 245-247, 250-251
 - in circuit averaged models, 237-238
 - comparison with DCM model, 377
 - derivation of, 40-43
 - equivalence with dependent sources, 41
 - manipulation of circuits containing, 41-42, 48-49

- in a nonideal boost converter, 48-49, 56
 - in a nonideal buck converter, 52-53
 - in small-signal ac CCM models, 208-210
- Decibel, 262
- Delta-wye transformer connection, 582-583
- Dependent power source (*see* Power source element)
- Derating factor, 180
- Design-oriented analysis, techniques of
- analytical expressions for asymptotes, 275-276
 - approximate factorization, 285-288
 - doing algebra on the graph, 296-309
 - frequency inversion, 271-272
 - graphical construction
 - of Bode plots, 296-309
 - of closed-loop transfer functions, 329-332
 - low Q approximation, 282-284
 - philosophy of, 261, 306-307
- Differential connection of load
- polyphase inverter, 143-148
 - single-phase inverter, 142-143
- Diode
- antiparallel, 67
 - characteristics of, 78
 - fast recovery, 77
 - forward voltage drop (*see also* Semiconductor conduction losses), 53-57, 77
 - freewheeling, 67
 - parallel operation of, 77-78
 - recovered charge Q_r , 76, 97-100, 692, 729
 - recovery mechanisms, 76-77, 98-100
 - Schottky, 74, 77, 101
 - soft recovery, 98-99
 - snubbing of, 99
 - switching loss, 97-100, 101-103, 692
 - switching waveforms, 75-77, 98-100, 101-102
 - zero current switching of, 101-103, 690-692, 696, 725-726
 - zero voltage switching of, 692-696, 725-726, 729, 734
- Discontinuous conduction mode (DCM)
- B - H loop, effect on, 503-504
 - boost converter example, 121-127
 - buck converter example, 111-121
 - buck-boost converter example, 370-381
 - in current programmed converters, 438-447
 - equivalent circuit modeling of, 369-381, 438-444
 - in forward converter, 159
 - in line-commutated rectifiers, 564-568, 569-570
 - in low-harmonic rectifiers
 - boost rectifier, single phase, 594-597
 - single-switch, three-phase, 615-619
 - mode boundary
 - in boost rectifier, 594-697
 - vs. K , 111-115, 121-122, 128
 - vs. load current and R_e , 381
 - origin of, 111-115
 - in parallel resonant converter, 687-689

- in PWM converters, 110-134, 369-407, 438-447
 - in series resonant converter, 681-683
 - small-signal ac modeling of, 382-403
- Displacement factor, 548, 550-551
- Distortion factor (*see also* Total harmonic distortion), 548-550
- of single-phase rectifier, 548, 563-566
- Distributed power system, 9
- Doing algebra on the graph (*see* Graphical construction of Bode plots)
- Duty ratio
- complement of, 16
 - definition of, 15-16
- EC core data, 754
- Eddy currents
- in magnetic cores, 472
 - in winding conductors, 474-477
- EE core data, 753
- Effective resistance R_e
- in DCM averaged switch model, 374-381
 - in loss-free resistor model, 374-381
 - in resonant converter models
 - with capacitive filter network, 666-668
 - with inductive filter network, 674-676
- Emulated resistance R_e , 590-593
- Efficiency, 2
- averaged switch modeling, predicted by, 245
 - of boost converter
 - as low-harmonic rectifier, 632-634
 - nonideal dc-dc, 49-51, 56
 - calculation via averaged model, 49-51, 56
 - vs. switching frequency, 103-104
- Equivalent circuit modeling
- by canonical circuit model, 245-251
 - of CCM converters operating in steady-state, 40-61
 - of converters having pulsating input currents, 51-53
 - of current programmed switch networks
 - CCM, 423-428
 - DCM, 438-447
 - small-signal models, 421-422, 423-428, 445-447
 - of flyback converter, CCM, 168, 216-218
 - of ideal rectifiers, 590-593, 608-611
 - of ideal dc-dc converters, 40-42
 - of inductor copper loss, 43-51
 - small-signal models
 - CCM, 207-209, 230-232
 - DCM, 382-390
 - current programmed, 421-422, 424-428, 438-447
 - of switching loss, 241-245
 - of switch networks
 - CCM, 239-242
 - DCM, 370-381
 - of systems containing ideal rectifiers, 602
- Equilibrium (*see* Steady state)
- Equivalent series resistance (esr) of capacitor, 554-555
- ETD core data, 754

- Evaluation and design of converters, 177-183
- Experimental techniques
 - measurement of impedances, 312-314
 - measurement of loop gains
 - by current injection, 359-360
 - by voltage injection, 357-359
 - of an unstable system, 360-361
 - measurement of small-signal transfer functions, 309-311
- Factorization, approximate
 - approximate roots of arbitrary-degree polynomial, 282-288
 - graphical construction of Bode diagrams, 296-309
 - low- Q approximation, 282-284
- Faraday's law, 456-457
- Feedback (*see* Control system design, Negative feedback)
- Ferrite
 - applications of, 499, 525, 528
 - core loss, 472, 473-474, 518
 - core tables, 751-755
 - saturation flux density, 459, 473
- Fill factor (*see* K_u)
- Filter inductor
 - B - H loop of, 497, 499
 - design of
 - derivation of procedure, 503-508
 - step-by-step procedure, 508-509
- Flux Φ , 456
- Flux density B
 - definition, 456
 - saturation value B_{sat} , 458-459
- Flux-linkage balance (*see* Inductor volt-second balance)
- Flyback converter (*see also* Buck-boost converter)
 - active switch utilization, 178-179
 - derivation of, 166-167
 - nonideal, ac modeling of, 209-218
 - single-switch rectifier, 3 ϕ ac-dc DCM, 623
 - spreadsheet design example, 180-183
 - steady-state analysis of, 166-170
 - two transistor version, 185-186
 - utilization of flyback transformer, 170-171
- Flyback transformer, 166-167, 170-173, 502-503, 619
- Forced commutation of SCRs, 90
- Forward converter (*see also* Buck converter), 159-164
 - active switch utilization, 179
 - spreadsheet design example, 180-183
 - steady-state analysis of, 159-164
 - transformer reset mechanisms, 162-163
 - transformer utilization in, 164
 - two transistor version, 163-164
- Four-quadrant switches (*see* Switch)
- Freewheeling diode, 67
- Frequency modulator, 732-733
- Gate turn-off thyristor (GTO), 92
- Generalized switch averaging, 390-403

- Geometrical constant (*see* K_g , K_{gfe})
- Graphical construction of Bode plots (*see also* Bode plots, Design-oriented analysis)
 - of converter transfer functions, 307-309
 - division, 307-309
 - of harmonic trap filters, 576-582
 - parallel combinations, 301-307
 - parallel resonance, 301-303
 - of parallel resonant converter, 677
 - series combinations, 296-301
 - series resonance, 298-301
 - of series resonant converter, 671-672
- Grounding problems, 312-314
- Gyrator, 682-683
- Harmonic correction, 621
- Harmonic loss factor F_H , 488-490
- Harmonics in power systems
 - average power vs. Fourier series, 542-543
 - distortion factor, 548
 - harmonic standards, 555-559
 - neutral currents, 552-553
 - power factor, 546-550
 - root-mean-square value of waveform, 543-546
 - rectifier harmonics, 548-550
 - in three-phase systems, 551-555
 - total harmonic distortion, 548
- Harmonic trap filters, 575-582
 - bypass resistor, 580-582
 - parallel resonance in, 577-579
 - reactive power in, 582
- H-bridge, 7-8, 142-145, 148-150
- Hold-up time, 601
- Hot spot formation, 77-78, 85-86
- Hysteresis loss P_H , 471-472
- Hysteretic control, 639-641
- Ideal rectifier (*see also* Low harmonic rectifiers), 590-626
 - in converter systems, 599-604
 - properties of, 590-593
 - realization of
 - single phase, 593-599
 - three phase, 608-622
 - rms values of waveforms in, 604-608
- IEC-555, 556-557
- IEEE/ANSI standard 519, 557-559
- Impedance graph paper, 307
- Inductor copper loss (*see* Copper loss)
- Inductor current ripple
 - in ac inductor, 499-500
 - boost example, 28
 - buck example, 21
 - calculation of, 21
 - in converters containing two-pole filters, 34-36
 - Cuk converter example, 32-33
 - in filter inductor, 497-499

- magnitude vs. DCM, 111-113
- Inductor design
 - ac inductor design
 - derivation, 531-533
 - step-by-step procedure, 533-534
 - filter inductor design
 - derivation, 503-508
 - step-by-step procedure, 508-509
- Inductor volt-second balance
 - boost example, 25-26
 - buck example, 22-23
 - Cuk converter example, 31-32
 - definition, 22
 - in discontinuous conduction mode, 115
- Input port, converter
 - ac modeling of, 203
 - boost static characteristics, 596-597, 639
 - modeling of, via state-space averaging, 200, 227, 231
 - steady-state modeling of, 51-53
- Inrush current, 601-602
- Insulated-gate bipolar transistor (IGBT)
 - construction and operation of, 87-90
 - current tailing in, 88-89, 96-97
 - equivalent circuit, 88
 - forward voltage drop, modeling of, 89
 - idealized switch characteristics, 65-66
 - parallel operation of, 89
 - switching loss in, 96-97
- Inversion of source and load, 136-137
- Inverters, 1
 - high frequency, 659-662, 697-705
 - line commutated, 572-573
 - single phase, 7-8, 68-69
 - sinusoidal analysis of resonant converters, 664-670, 697-705
 - three phase, 70, 143-148
- Iron laminations, 459, 473
- K , dimensionless parameter
 - critical value $K_{crit}(D)$, 114-115, 121-122, 128
 - in current programmed mode analysis, 438
 - and DCM boundary, 114-115, 121-122, 128
 - in line-commutated rectifier analysis, 565-566
 - in steady-state DCM analysis, 120, 127-128
- K_g , core geometrical constant
 - definition of, 507-507, 751
 - ferrite core tables of, 752-755
 - filter inductor design procedure using, 508-509
- K_{ge} , ac core geometrical constant
 - ac inductor design procedure using, 531-534
 - definition of, 521, 751
 - ferrite core tables of, 752-755
 - transformer design using,
 - derivation, 517-521
 - examples, 524-531
 - step-by-step procedure, 521-524

- K_L , rectifier dimensionless parameter, 565-566
- K_u , window utilization factor, 507
- LCC resonant converter
 - dependence of transistor current on load, 701-702
 - introduction to, 659-661
 - ZVS/ZCS boundary, 703-705
- Lenz's law, 457, 472, 475
- Linear ripple approximation (*see* Small ripple approximation)
- Line-to-output transfer function $G_{vg}(s)$
 - of the buck, boost, and buck-boost converters in CCM, 292-293
 - canonical model, as predicted by, 247-248
 - closed-loop, 326-327, 331-332
 - control system design of, 340, 353-354
 - of current-programmed converters, 422, 427-428, 437-438
 - of DCM converters, 387-388
 - of quasi-resonant converters, 736
- Litz wire, 487
- Loop gain (*see also* Control system design, Negative feedback)
 - definition, 327
 - measurement of, 355-361
- Loss-free resistor model
 - averaged switch model of discontinuous conduction mode, 374-381
 - ideal rectifier model
 - single phase, 590-593
 - three phase, 608-611
- Low harmonic rectifiers (*see also* Ideal rectifiers)
 - controller schemes
 - average current control, 634-636
 - current programmed control, 636-640
 - feedforward, 635-636
 - hysteretic control, 639-641
 - nonlinear carrier control, 641-645
 - modeling of
 - efficiency and losses, 627-634
 - low-bandwidth control loop, 645-650
 - wide-bandwidth average current control loop, 650-652
 - rms calculations in, 604-609
- Low Q approximation, 282-284
- Magnetic circuits, 463-466
- Magnetic field H , 455-456
- Magnetic path length l_m
 - definition, 461
 - ferrite core tables, 752-755
- Magnetics, 453-538
 - ac inductor design, 531-534
 - basic relations, 455-462
 - copper loss, 474
 - core loss, 471-474
 - ferrite core tables, 752-755
 - filter inductor design, 503-509
 - magnetic circuits, 463-466
 - magnetic devices, types of, 497-503
 - optimizing B_{max} to minimize total loss, 520-521
 - optimizing window allocation to minimize copper loss, 513-517

- proximity effect, 476-490
- transformer basics, 152-154, 466-471
- transformer design, 517-531
- Magnetizing current, 152-153, 458-469
- Magnetomotive force (MMF)
 - definition, 455-456
 - MMF diagrams, 479-482
- Majority carrier devices (*see also* MOSFET, Schottky diode), 74-75
- Matrix converter, 72-73
- Mean length per turn (*MLT*)
 - definition, 507-508
 - ferrite core tables, 752-755
- Measurement of transfer functions and loop gains (*see* Experimental techniques)
- MIL-STD-461B, 556
- Minority carrier devices (*see also* Bipolar junction transistor, Diode, Gate turn-off thyristor, Insulated-gate bipolar transistor, MOS-controlled thyristor, Silicon controlled rectifier), 74-75
- Modulation index, 613-614
- MOS-controlled thyristor (MCT), 92-94
- MOSFET
 - body diode, 67-68, 79-80
 - conduction loss, modeling of, 53-57, 209-218
 - construction and operation of, 78-82
 - on resistance, 53-57, 79-82
 - switching loss owing to C_{ds} , 100-101
 - as synchronous rectifier, 73-74
 - terminal capacitances, 81
 - typical characteristics, 80-82
 - zero-voltage and zero-current switching of, 689-696
- Motor drive system, 9-10
- Multiplying controller (*see also* Average current control, Current programmed control), 596
- Multi-resonant switch
 - single-switch 3 ϕ buck rectifier, 620-621
 - zero-voltage switching dc-dc, 729
- Negative feedback (*see also* Control system design)
 - effects of, on network transfer functions, 326-329
 - objectives of, 193-194, 323-326
 - reduction of disturbances by, 327-329
 - reduction of sensitivity to variations in forward gain by, 329
- Nonlinear carrier control, 641-645
- Nonminimum-phase zero (*see* Right half-plane zero)
- Output characteristics
 - of the parallel resonant converter, 689
 - of resonant inverters, 699-700
 - of the series resonant converter, 685-686
- Overshoot, 338-340
- Parallel resonant converter
 - analysis via sinusoidal approximation, 664-670, 674-678
 - dependence of transistor current on load, 702
 - exact characteristics
 - continuous conduction mode, 686-687
 - control plane, 689
 - discontinuous conduction mode, 687-689
 - output plane, 689

- introduction to, 659-660
- as a low harmonic rectifier, 597
- Permeability μ
 - definition, 458-460
 - of free space, μ_0 , 458
 - relative, μ_r , 458
- Phase asymptotes
 - of complex poles, 279-282
 - inverted forms, 272
 - of real pole, 266-268
 - of real zero, 269
 - of RHP zero, 270
- Phase control
 - of resonant converters, 659
 - of three-phase rectifiers, 570-575
 - of zero-voltage transition dc-dc converter, 696
- Phase margin
 - vs. closed-loop damping factor, 334-338
 - stability test, 333-334
- Poles
 - complex, Bode plots of, 276-282
 - the low Q approximation, 282-284
 - real, Bode plots of, 263-268
- Pot core data, 752
- Powdered iron, 459, 473
- Power factor (*see also* Total harmonic distortion, Displacement factor, Distortion factor)
 - definition of, 546-550
 - of bridge rectifier, single phase, 566
 - of peak detection rectifier, 548-550
 - of phase-controlled rectifier, three phase, 573
- Power sink element (*see* Power source element)
- Power source element
 - in averaged switch models
 - current programmed mode, CCM, 423-428
 - current programmed mode, DCM, 438-447
 - discontinuous conduction mode, 370-382
 - definition of, 375-377
 - in ideal rectifier model, 592, 599-603, 608-610
 - linearization of, 384-385, 425-426
 - in loss-free resistor model, 376-379
 - properties of, 375-377
- PQ core data, 755
- Proximity effect
 - conductor spacing factor η , 478
 - interleaving, effect on, 485-487
 - layer copper loss, 482-483
 - Litz wire, effect of, 487
 - MMF diagrams, 479-482
 - PWM waveform harmonics, 487-490
 - simple explanation, 476-478
 - transformer design procedure, accounting for, 519
 - winding loss, total, 483-487

- Pulse width modulation (PWM), 6-8, 17
 - modulator ac model, 253-254
 - operation of modulator, 252
 - spectrum of PWM waveform, 194-195
- Push-pull isolated converters
 - based on boost converter, 173
 - based on buck converter, 164-166, 410
 - Watkins-Johnson converter, 173
- Q factor, 277-282
 - canonical model, predicted by, 309
 - closed-loop, vs. phase margin, 334-338
 - of the CCM buck, boost, and buck-boost converters, 293
 - the low Q approximation, 282-284
 - vs. overshoot, 338-339
 - of parallel resonant circuit, 303
 - of series resonant circuit, 300-301
- Quasi-resonant converters (*see also* Multi-resonant switch, Quasi-square-wave switch)
 - ac modeling of, 732-737
 - single-switch 3ϕ buck rectifiers
 - multi-resonant, 620-621
 - zero current switching, 619-620
 - zero-current switching dc-dc
 - full wave, 723-724
 - half wave, 713-723
 - zero-voltage switching dc-dc, 726-728
- Quasi-square-wave converters, 730-731
- Quasi-static approximation, 661
- Quiescent operating point, 196-197, 204, 225
- Reactance graph paper (*see* Impedance graph paper)
- Reactive power
 - definition, 550-551
 - in harmonic trap filters, 582
 - in phase-controlled rectifiers, 573
- Rectifiers (*see also* Ideal rectifiers, Low harmonic rectifiers), 1
 - energy storage in single-phase, 599-604
 - high quality, 541
 - ideal, 590-626
 - line-commutated
 - phase control of, 570-575
 - single-phase, 548-550, 562-568
 - three-phase, 568-575
 - three-phase transformer connections in, 582-584
 - twelve pulse, 582-584
 - in resonant dc-dc converter, 666-668, 674-676
- Regulator system (*see also* Control system design), 192-193, 323-326, 634-645
- Reluctance, 463-466
- Resonance
 - Bode plots of complex poles, 276-282
 - graphical construction examples, 296-309
 - the low- Q approximation, 282-284
 - parallel resonant network, 301-307
 - series resonant network, 301-307
- Resonant converters (*see also* Quasi-resonant converters, Multi-resonant converters, Quasi-square-wave converters, Zero voltage transition converter), 659-710

- analysis of, via sinusoidal approximation, 664-679
 - LCC, 659-661, 701-705
 - parallel, 597, 659-660, 674-678, 686-690, 702
 - resonant link, 662
 - series, 659-674, 679-686, 690-695, 702
- Resonant link converters, 662
- Resonant switches (*see* Quasi-resonant converters, Multi-resonant switch, Quasi-square-wave converters)
- Right half-plane zero
- Bode plot of, 269-271
 - physical origins of, 294-295
- Ripple, switching, 17-19, 111-113, 194-196
- Root mean square value
- of commonly-observed converter waveforms, 743-750
 - vs. Fourier series, 543-546
 - of near-ideal rectifier currents, table of, 609
 - of near-ideal rectifier waveforms, 604-609
- Rotation of three-terminal cell, 141-142
- Saturation
- of inductors, 462, 465-466
 - of magnetic materials, 458-460
 - of transformers, 153-154, 469
- Schottky diode, 74, 77, 101
- Semiconductor conduction loss
- boost converter example, 53-57
 - inclusion in ac model, 209-218
 - with synchronous rectifier, 73-74
- Semiconductor cost, 180
- Semiconductor power devices (*see also* Bipolar junction transistor, Diode, Gate turn-off thyristor, Insulated-gate bipolar transistor, MOS-controlled thyristor, Schottky diode, Silicon controlled rectifier), 62-109
- charge control of, 75, 83-85, 94, 98, 101-103
 - conductivity modulation, 75
 - majority vs. minority carriers, 74-75
 - realization of switches using, 62-74
- SEPIC (*see* Single-ended primary inductance converter)
- Series pass regulator, 4-5
- Series resonant converter
- analysis via sinusoidal approximation, 664-674
 - dependence of transistor current on load, 702
 - exact characteristics
 - continuous conduction mode, 679-681
 - control plane, 684
 - even discontinuous conduction mode, 682
 - odd discontinuous conduction mode, 681
 - output plane, 685-686
 - introduction to, 659-664
 - subharmonic modes in, 673-674
 - zero-current switching in, 690-692
 - zero-voltage switching in, 692-695
- Silicon area (*see* Switch stress)
- Silicon controlled rectifier (SCR)
- construction and characteristics of, 89-92
 - equivalent circuit, 90

- inverter grade, 91
- Silicon steel, 459, 473
- Single-ended primary inductance converter (SEPIC), 38, 148
 - averaged switch model of
 - continuous conduction mode, 757-762
 - discontinuous conduction mode, 379-381
 - conversion ratio $M(D)$, 151, 381
 - inverse of, 151, 176
 - as low-harmonic rectifier, 597-599, 608-609
 - transformer isolation in, 174-176
- Single quadrant switch
 - definitions, 63-64
 - implementation, 64-67
 - origins of DCM, 110-113
- Sinusoidal approximation, 663, 664-679
- Sinusoidal PWM, 612-614
- Skin effect (*see also* Proximity effect), 472-476
- Slope compensation (*see* Artificial ramp)
- Small ripple approximation
 - in ac modeling approach, 198, 223-224
 - and average power loss, prediction of, 57
 - boost example, 25
 - buck example, 20
 - Cuk converter example, 30-31
 - definition, 19
 - in discontinuous conduction mode, 116
 - failure of, in two-pole filters, 34-36
- Small-signal ac modeling
 - via averaged switch modeling, 239-245
 - via circuit averaging, 231-245
 - of CCM converters, 193-260
 - of current programmed converters, 418-447
 - of DCM converters, 382-403
 - via generalized switch averaging, 390-403
 - of low harmonic rectifiers, 645-652
 - of quasi-resonant converters, 732-737
 - of resonant converters, 678
 - via state-space averaging, 218-231
- Snubber networks, 86, 94, 99, 696
- Soft switching (*see also* Zero current switching, Zero voltage switching), 689-696
- Spacecraft power system, 9
- Spreadsheet design of converters, 180-183
- State equations of a network, 218-221
- State-space averaging, 218-231
 - discussion, 223-226
 - example: nonideal buck-boost converter, 227-231
 - summary of result, 221-222
- Steady state
 - inductor current waveform, 22
 - operating point, 196-197, 204, 225
- Subharmonic
 - modes of series resonant converter, 673-674
 - number ξ , 679

Switch

- averaged modeling of, 239-245, 377, 390-403
 - current-bidirectional two-quadrant, 67-70
 - four-quadrant, 71-73
 - ideal SPDT in converters, 4-6, 15-16, 24, 29
 - ideal SPST, 62-63
 - passive vs. active, 64-65, 91
 - power dissipated by ideal, 6, 17
 - quasi-resonant, 711-737
 - realization of, using semiconductor devices, 62-74
 - single-quadrant, 64-67
 - synchronous rectifier, 73-74
 - voltage-bidirectional two-quadrant, 70-71
- Switch conversion ratio μ
- definition, 392
 - DCM buck example, 395-401
 - in generalized canonical model, 405
 - of multi-resonant switch, 729
 - of quasi-resonant switches
 - full-wave ZCS, 723-724
 - full-wave ZVS, 727
 - half-wave ZCS, 713, 720-721
 - half-wave ZVS, 727
 - small-signal ac modeling using, 732-737
 - of quasi-square-wave switches, 731
- Switched mode, 3-4
- Switching frequency
- converter efficiency vs., 103-104
 - definition of, 16
 - transformer size vs., 527
- Switching harmonics (*see also* Ripple, switching), 6
- removal of via averaging, 194-196
- Switching loss (*see also* Soft switching, Zero current switching, Zero voltage switching)
- averaged switch modeling of, 241-245, 259-260
 - with clamped inductive load, 94-97
 - and current tailing, 96-97
 - and device capacitances, 100-101
 - and diode recovered charge, 97-100, 101-103
 - effect on converter efficiency, 103-104
 - and ringing waveforms, 101-103
 - and stray inductances, 100-101
- Switch stress S , 177-180
- Switch utilization U , 177-180
- Synchronous rectifier, 73-74
- Temperature rise
- in a converter, 2
 - in magnetics, 752
- Thyristor (*see* Gate turn-off thyristor, MOS-controlled thyristor, Silicon controlled rectifier)
- Topologies of converters (*see also* Boost, Bridge configuration, Buck, Buck-boost, Cuk converter, Forward converter, Transformer-isolated converters, etc.)
- Cascade connections, 138-141
 - Converter synthesis, 146-150

- Differential connection of load, 142-146
- Evaluation and comparison, 177-183, 608-609
- Inversion of source and load, 136-137
- Low-harmonic single-phase rectifiers, 593-599
- Low-harmonic three-phase rectifiers, 608-621
- Quasi-resonant converters, 724-731
- Resonant converters, 659-664
- Rotation of three-terminal cell, 141-142
- Transformer isolation, 150-177
- Total harmonic distortion (THD)
 - of current-programmed rectifiers, 639
 - definition, 550
 - vs. distortion factor, 550-551
 - IEEE-519 limits, 559-561
 - of peak detection rectifier, 551-552
 - of single-phase bridge rectifiers, 551-552, 566-570
 - of three-phase bridge rectifiers, 571-572, 575
- Transfer functions (*see also* Bode plots)
 - of the buck, boost, and buck-boost converters, 292-293
 - of current programmed converters, 422-423, 427, 436-438, 446-447
 - of DCM converters, 388-390
 - graphical construction of, 296-309
 - of low-harmonic rectifiers, 649-650, 651
 - measurement of, 309-311
 - predicted by canonical model, 247-248, 292-293
- Transformer connections in three-phase rectifiers, 582-584
- Transformer-isolated converters, 150-177
 - boost-derived topologies, 171-173
 - Cuk converter, 176-177
 - evaluation and comparison of, 177-183
 - flyback, 166-171
 - forward, 159-164
 - full bridge buck-derived, 154-157
 - half-bridge buck-derived, 157-159
 - multiple outputs and cross regulation, 151-152
 - push-pull buck-derived, 164-166
 - SEPIC, 174-176
 - transformer model, 152-154, 466-471
 - use of volt-second balance in, 153-154, 156-157
- Transformers
 - B-H* loop in, 153, 500-501
 - design of,
 - derivation of procedure, 517-521
 - examples, 524-531
 - step-by-step procedure, 521-524
 - winding area optimization, 513-517
 - flyback transformer, 166-167
 - leakage inductance, 154, 469-471
 - magnetizing inductance, 152-154, 468-469
 - modeling of, 152-154, 466-471
 - SEPIC transformer, 174-175
 - volt-second balance in, 153-154, 156-157
- Triplen harmonics
 - in three-phase four-wire networks, 552-553

- in three-phase inverter modulation schemes, 614
- in three-phase rectifier circuits, 568-569
- in three-phase three-wire networks, 553-554
- Twelve-pulse rectifier, 582-584
- Two-quadrant switches (*see* Switch)
- Universal-input rectifiers, 602
- Variable-speed ac drive, 7-8
- Voltage conversion ratio (*see* Conversion ratio M)
- Voltage injection, 357-359
- Voltage-source inverter, 70, 146-147
- Volt-second balance (*see* Inductor volt-second balance)
- Watkins-Johnson converter, 148, 150, 173
 - inverse of, 148, 150
 - isolated push-pull, 173
- Window area W_A
 - allocation of, to minimize total copper loss, 513-517
 - definition, 506-507
 - ferrite core tables, 752-755
- Window utilization factor K_u , 507
- Wire area A_w
 - inductor design, 506-507, 509
 - American wire gauge (AWG) table, 755-756
- Zero-current switching (ZCS), 662
 - in quasi-resonant converters, 712-726
 - in quasi-square-wave converters, 730-731
 - in series resonant converter, 690-692
 - in single-switch three-phase low-harmonic rectifiers, 619-621
 - ZCS/ZVS boundary, 702-705
- Zero-voltage switching (ZVS), 662
 - in LCC resonant converter, 703-705
 - in multi-resonant converters, 729
 - in quasi-resonant converters, 726-728
 - in quasi-square-wave converters, 730-731
 - in series resonant converter, 692-695
 - in single-switch three-phase low-harmonic rectifiers, 619-621
 - in zero-voltage transition converter, 695-696
 - ZVS/ZCS boundary, 702-705
- Zero-voltage transition buck-derived converter, 695-696