Figure 1

This SOT-23 IC with low-cost external components provides a combination of power-on reset and an efficient logic supply.